


EXPERIMENT 2 PARALLEL RESONANCE (Complex impedance.)

PURPOSE:

To study the dependence of impedance as a function of frequency when capacitors and inductors are connected in parallel.

THEORETICAL CONSIDERATIONS:

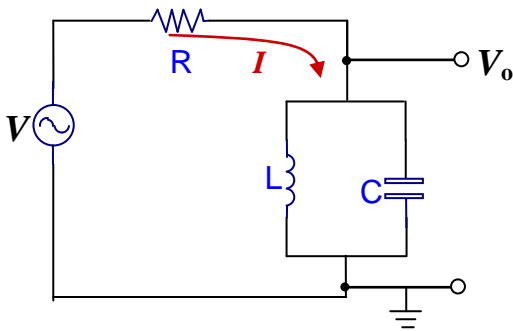Similar to the series connection counterpart, resonance also occurs in a RLC parallel circuit. In the former, the current peaks at the resonance frequency; in the latter, the voltage across the inductor or the capacitor is the quantity that peaks. To analyze the circuit, let's calculate the impedances and current across the circuit.



- The impedance Z_1 across the inductance and the capacitor (connected in parallel) is calculated through the expression,

$$\frac{1}{Z_1} = \frac{1}{j\omega L} + \frac{1}{1/(j\omega C)} = \frac{1 - \omega^2 LC}{j\omega L}. \text{ Hence,}$$

$$Z_1 = j \frac{\omega L}{1 - \omega^2 LC} \quad (\text{across LC}) \quad (1)$$

Notice, this impedance is very large when

$$\omega = \omega_o = \frac{1}{\sqrt{LC}}$$

The total impedance of the circuit is: $Z = R + j \frac{\omega L}{1 - \omega^2 LC}$ (2)

- For an applied harmonic voltage $V = V_p e^{j\omega t}$ the resulting total current is:

$$I = \frac{V}{R + j \frac{\omega L}{1 - \omega^2 LC}} \quad (3)$$

Notice the current is zero at resonance (where the impedance becomes infinity.)

- The voltage V_o is equal to $I Z_1$,

$$V_o = I Z_1 = \frac{V}{R + j \frac{\omega L}{1 - \omega^2 LC}} \frac{j\omega L}{1 - \omega^2 LC} = \frac{j\omega L}{R(1 - \omega^2 LC) + j\omega L} V$$


An equivalent expression can be worked out for V_o .

$$V_o = \frac{1 + j(R/\omega L)(1 - \omega^2 LC)}{1 + (R/\omega L)^2 (1 - \omega^2 LC)^2} V \quad (4)$$

A relationship between the magnitudes of and results,

$$\left| \frac{V_o}{V} \right| = \frac{1}{\sqrt{1 + (R/\omega L)^2 (1 - \omega^2 LC)^2}}$$

(5)

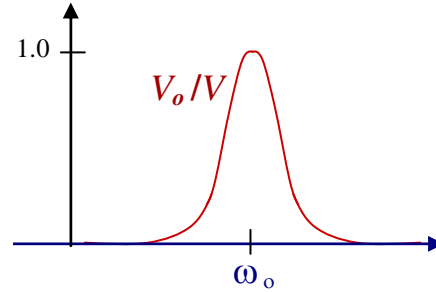

At $\omega = \omega_o \equiv \frac{1}{\sqrt{LC}}$:

- The current I is zero
- The output voltage V_o across the LC combination becomes equal the input voltage V , independent of the value of R .
- The currents along the capacitor and inductance are $I_C = \frac{V}{1/(j\omega_o C)} = j\omega_o CV$ and

$I_L = \frac{V}{j\omega_o L} = -j\frac{1}{\omega_o L}V$, respectively. These two currents are equal in magnitude, but out of phase (they cancel each other so no current I passes through the resistor.) Accordingly, a circulating current exists in the parallel LC combination at resonance.

Parallel resonance is commonly used in electronic circuits to achieve a high impedance (which develops an appreciable signal at resonance.)


Parallel resonance is also used to emphasize a narrow frequency bandwidth over other frequency ranges: by changing the value of, for example, the capacitance, the circuit is tuned to different frequencies (radio, TV applications.)

EXPERIMENTAL CONSIDERATIONS:


The basic "signal generator" is the same as that used in Experiment-1. The oscilloscope connections are also the same initially.

MEASUREMENTS:

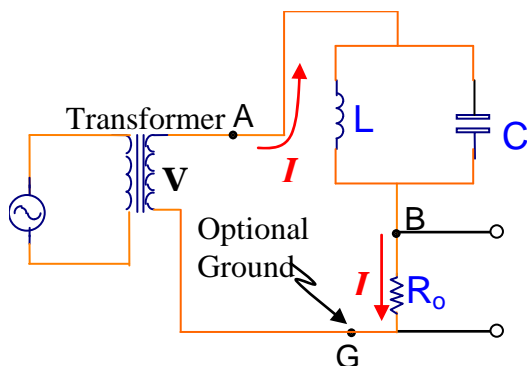- Take measurements similar to those of in Experiment-1 to determine the impedance for a circuit composed of the inductor and capacitor in parallel. Compare your results to theoretical predictions.




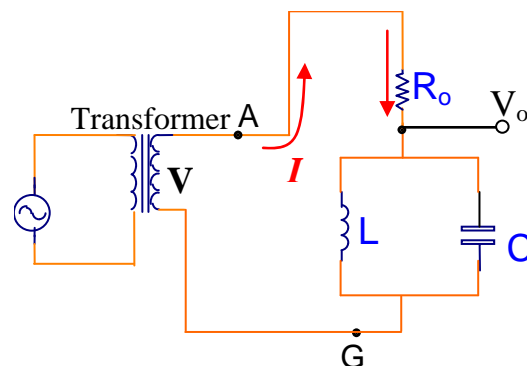Circuit for measuring V and I (hence, the impedance.)



Circuit for measuring V and V_o .

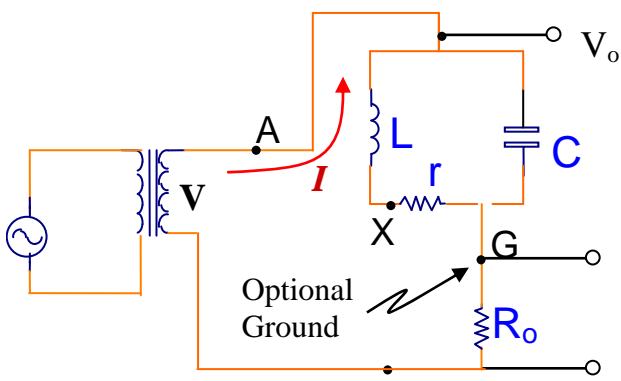In order to understand how the circuit operates more fully, it will be instructive to add the small resistor r . This will allow for several additional measurements:



- b) By shifting the oscilloscope input normally connected to A to point X, it will be possible to compare the amplitude and phase of the currents internal and external to the parallel resonance circuit for a variety of frequencies
- c) As additional measurements, you may wish to shift the resistor r to be in series with the capacitor instead.