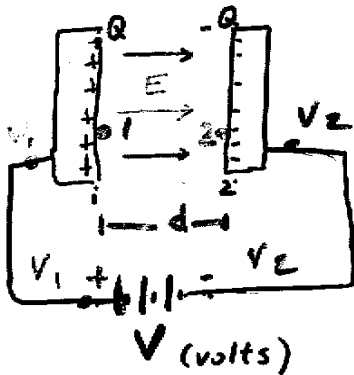


CAPACITANCE

Parallel-Plate Capacitor page 591




$$V_2 - V_1 = - \int_1^2 E \, dx$$

E is uniform between the parallel plates

$$= - E \int_1^2 dx = - E d$$

$$V_2 - V_1 = - E d$$

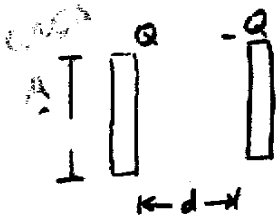this expression indicates that $V_1 > V_2$



Area of the plate

On the other hand, we already know E :

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q/A}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$V_1 - V_2 = E d$$

V (battery)



$$V = E d = \frac{Q}{\epsilon_0 A} d$$

$$\underbrace{\frac{\epsilon_0 A}{d}} V = Q$$


capacitance

$$Q = C V$$


capacitance

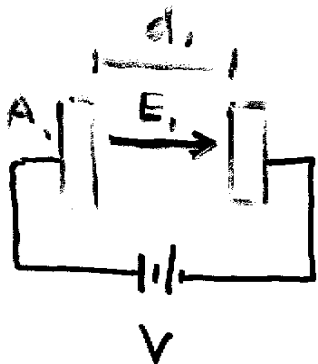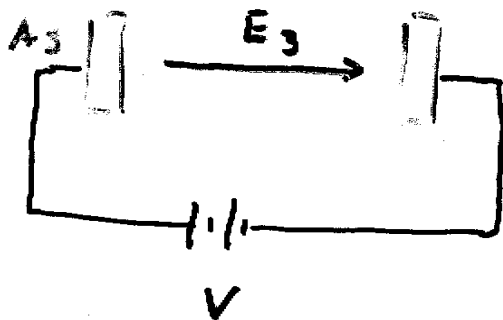 E_1 E_3 

$$A_1 = A_3$$

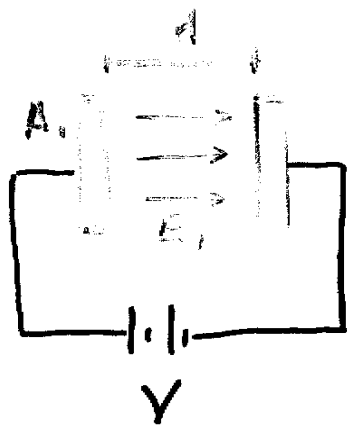

E_1 E_2

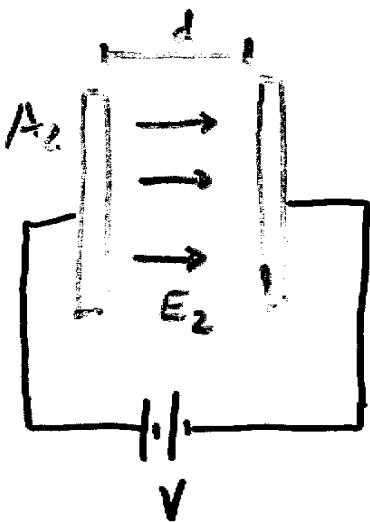

$A_2 > A_1$

$$Q = C V$$

↑
↑
↑
 electric potential difference

stored charge


capacitance
(value depends on the geometry of the electrodes)


For a parallel-plate capacitor:


$$C = \frac{\epsilon_0 A}{d}$$

unit 1 FARAD = 1F = $\frac{\text{coulomb}}{\text{volt}}$

We use capacitors to store charge:

step 1  Each plate is called "an electrode"
frontal view of 2 parallel plates

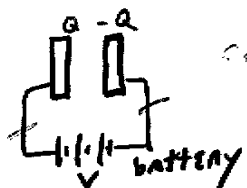step 2  connection to a battery

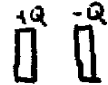step 3  after removing the battery, plates remained charged.

Notice: the higher the voltage, the more charge is deposited in the electrodes. $Q = CV$


* Exercise: Problems 2E, 5E, page 608
Chapter 26


Capacitors also store energy (electrical energy)

The question we are going to answer is
 "HOW MUCH ENERGY IS SPENT IN
 CHARGING A CAPACITOR"



Step 1  uncharged plates
 $C = \epsilon_0 A/d$

Step 2  Assume, at a given time, an amount of charge q has been transferred from the right plate to the left one.
 The potential difference between the plates is $V = \frac{q}{C}$

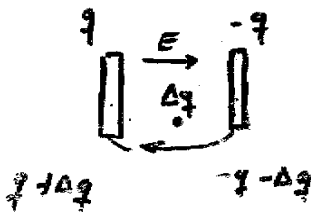Step 3  $\Delta W_{\text{ext}} = F_{\text{ext}} \cdot d = (\Delta q) E d = (\Delta q) V$
 external work required to transport a small charge Δq from the right plate to the left plate. $q = cV$

$$\Delta W_{\text{ext}} = V \Delta q = \frac{q}{C} \Delta q$$

$$W_{\text{ext}} = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \frac{q^2}{2} \Big|_0^Q$$

$$W_{\text{ext}} = \frac{1}{2} \frac{Q^2}{C}$$

EXTERNAL ENERGY
required to
charge a capacitor.

And, since $Q = CV$

$$W_{\text{ext}} = \frac{1}{2} CV^2$$

More common notation

$$U = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2$$


U : ^{POTENTIAL} ENERGY stored
in the capacitor.

QUESTION: Where is this energy U located?

Notice



before

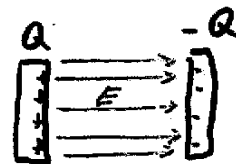

after

We may say that the energy U is distributed inside the volume of the plate capacitor.

We can further say that the energy U is stored in the electric field E

Some hints:

$$U = \frac{1}{2} C V^2 = \frac{1}{2} C (E d)^2 = \frac{1}{2} \epsilon_0 \frac{A}{d} \cdot (E d)^2$$

$$= \frac{1}{2} \epsilon_0 \underline{A d} E^2$$



$$\frac{U}{\text{volume}} = \frac{U}{A d} = \frac{1}{2} \epsilon_0 E^2 !$$

wherever there exist
an electric field E ,
there exist a
potential energy density


μ

$$\mu = \frac{1}{2} \epsilon_0 E^2$$


potential energy
per unit volume

"the electrical potential energy stored in the capacitor is considered to be stored in the electric field"

SEVERAL CAPACITORS CONNECTED IN SERIES

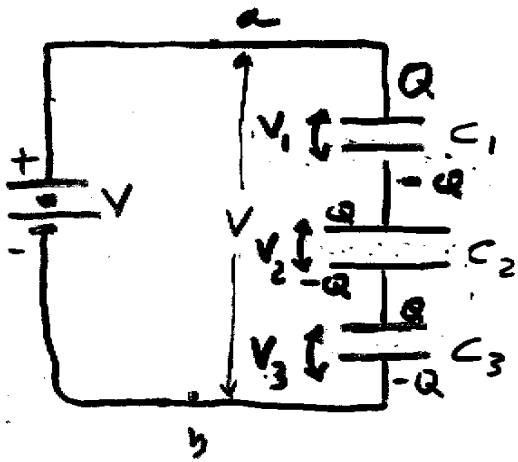

Equivalent
to

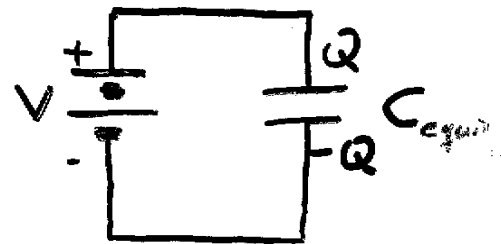

$C_{equiv} = ?$

$$V = V_1 + V_2 + V_3$$

$$Q = C_{equiv} V$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$



$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\Rightarrow \frac{1}{\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)} V = Q$$


C_{equiv}

$$C_{equiv} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$
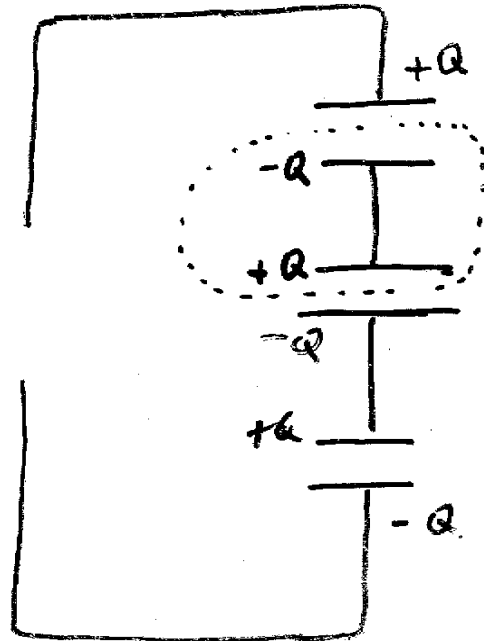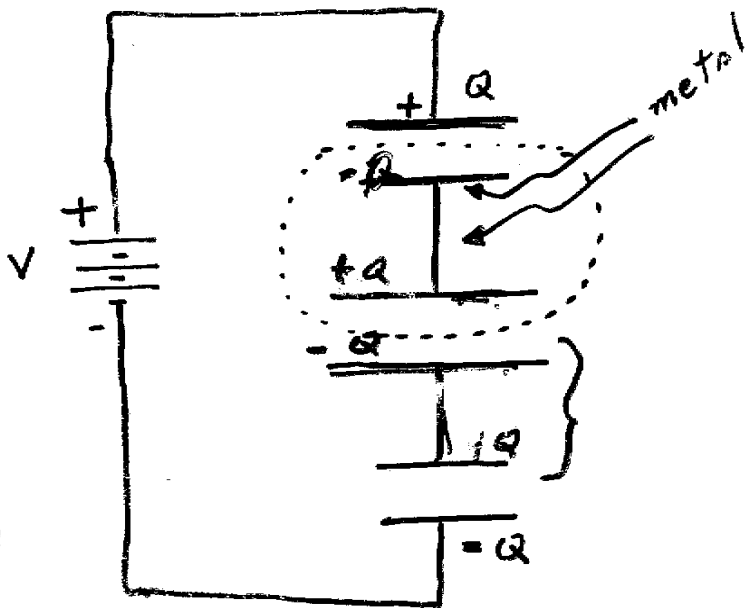
$$\frac{1}{C_{equiv}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



where: $C_1 \neq C_2 \neq C_3$

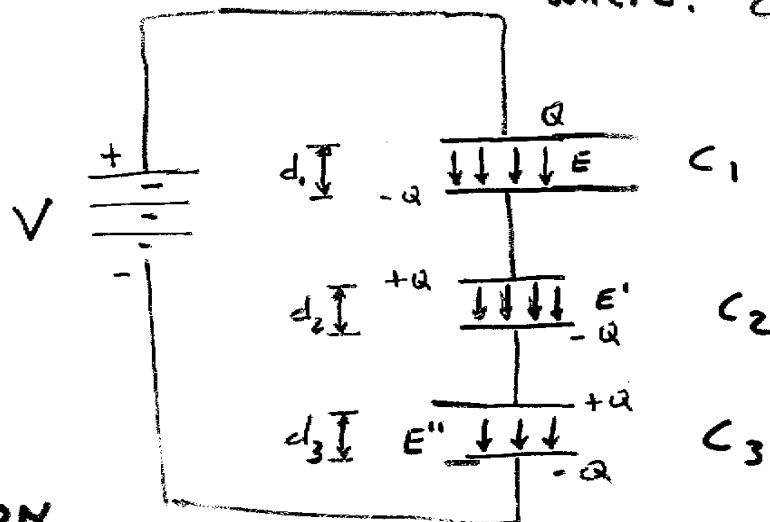


QUESTION


IS $E = E'$?
 $E' = E''$?

SEVERAL CAPACITORS CONNECTED IN PARALLEL . -

page 594

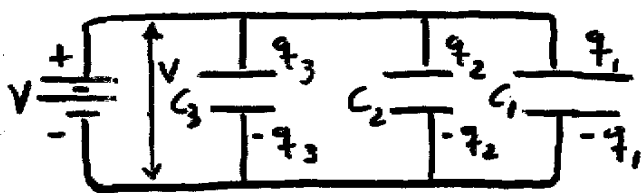
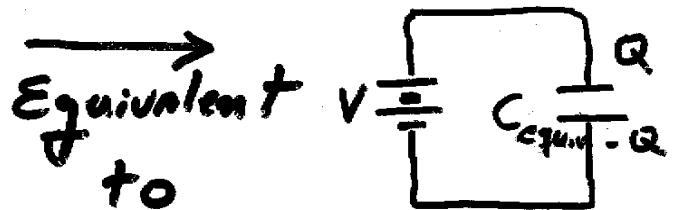
$$q_3 = C_3 V \quad q_2 = C_2 V \quad q_1 = C_1 V$$



$Q = C_{equiv} V$
For this circuit to be equivalent to the one in the left requires that

$$Q = q_1 + q_2 + q_3$$

Therefore :

$$Q = q_1 + q_2 + q_3 = C_1 V + C_2 V + C_3 V$$


$$\text{On the other hand} = V (C_1 + C_2 + C_3)$$

$$Q = C_{equiv} V$$

Which implies

$$C_{equiv} = C_1 + C_2 + C_3$$

C is the equivalent capacitance

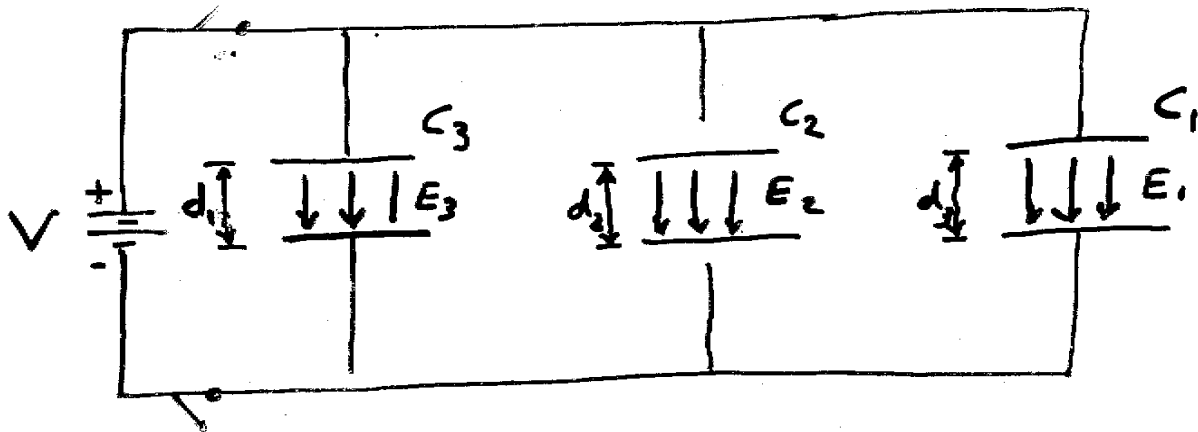

QUESTION: In the particular case that $d_1 = d_2 = d_3$, what can we say about E_1 , E_2 and E_3 ?

$$E_3 = E_2 ?$$

$$E_2 = E_1 ?$$

(Assume $C_1 \neq C_2 \neq C_3$)


SEVERAL CAPACITOR CONNECTED IN SERIES and PARALLEL.

Sample Problem 26-2.

(we'll do it on the blackboard)

* Sample problem 26-3, page 597


Step 1

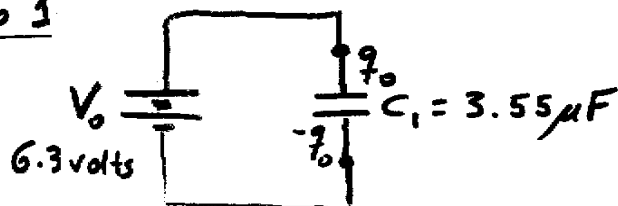

find how much
charge is stored
in the capacitor

$$q_0 = ? = C_1 V_0$$


Step 2 Battery removed

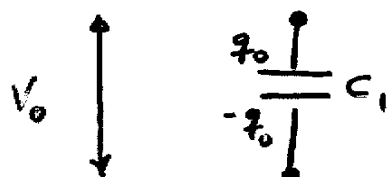

What is the potential
difference across the
capacitor?

$$V_0 = ? \quad 6.3 \text{ Volt}$$

STEP 3

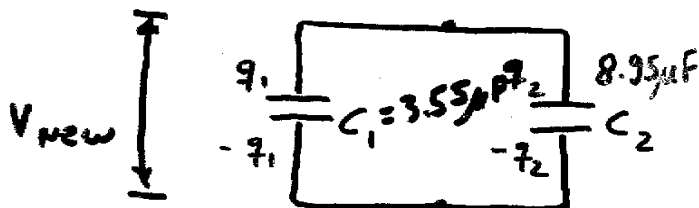

What is the
potential difference
across the
capacitors?

charge conservation indicates


$$\underbrace{q_0}_{\text{before}} = \underbrace{q_1 + q_2}_{\text{after}}$$

$$C_1 V_0 = C_1 V_{\text{new}} + C_2 V_{\text{new}}$$

$$\frac{C_1 V_0}{C_1 + C_2} = V_{\text{new}}$$

$$V_{\text{new}} = 1.79 \text{ V}$$


From step 2

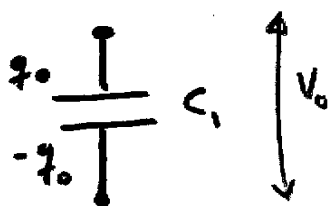

POTENTIAL ENERGY
STORED

$$U_i =$$

step 3

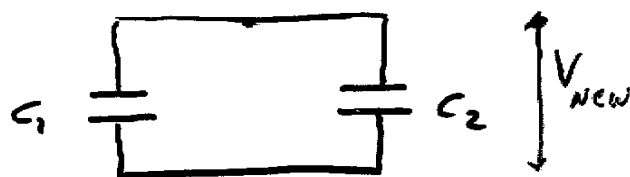

POTENTIAL ENERGY
STORED

$$U_f =$$

Q: Is there a violation of the conservation of ENERGY in this example?

$$U_i = \frac{1}{2} \frac{q_0^2}{C_1} = \frac{1}{2} \frac{(22.4 \mu\text{C})^2}{3.55 \mu\text{F}} = 70.45 \mu\text{J}$$

$$U_f = \frac{1}{2} \frac{q_1^2}{C_1} + \frac{1}{2} \frac{q_2^2}{C_2}$$

$$= \frac{1}{2} \frac{(C_1 V_{\text{new}})^2}{C_1} + \frac{1}{2} \frac{(C_2 V_{\text{new}})^2}{C_2}$$

$$= \frac{1}{2} \frac{(6.35 \mu\text{C})^2}{C_1} + \frac{1}{2} \frac{(16 \mu\text{C})^2}{C_2}$$

$$= 5.69 \mu\text{J} + 14.34 \mu\text{J}$$

Notice

$$U_f < U_i$$

final

initial

Extra curricular reading:

- Feynman, "Lectures on Physics", vol II

"The ambiguity of the field energy"
page 27-6


- No unique way to define U
neither where "exactly" is located.

- Possible solution: theory of gravitation

Theory of gravity says:

"all energy is source of
gravitational attraction"

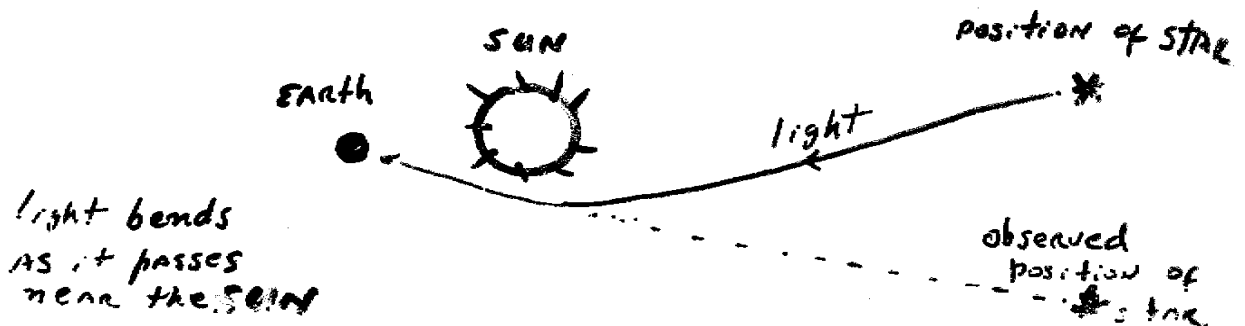therefore, this theory will require that
the energy-density of electricity
must be located properly as we
are to know in which direction
the gravity force acts.



EXTRA CURRICULAR READING:

- FEYNMAN LECTURES, VOL-II, CHAPTER 28
"ELECTROMAGNETIC MASS"


- Also, pages 19-11 to 19-14.
(about energy inside a capacitor)

* EXERCISE: Problems 23E and 24E, chapter 26,
page 609.

* Reading assignment: sample problem 26-2
" " 26-3

* Practice: Questions 4 and 9 (page 607)

CAPACITORS WITH A DIELECTRIC

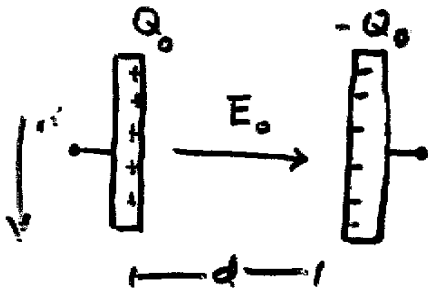


$$C_0 = \frac{\epsilon_0 A}{d}$$

$$V_0 = E_0 d$$

(capacitor was initially charged using battery. Then the battery was removed.)

⇒
inserting
a dielectric

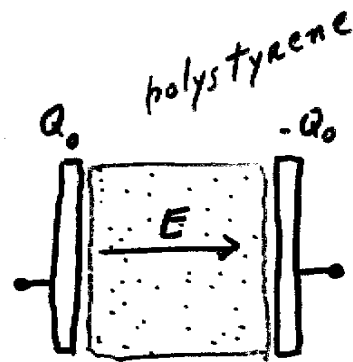

Experimentally it is found that the potential difference between the plates decreases

$$V = \frac{V_0}{K}$$

K : dielectric constant
(material property)

• what is the new electric field E ?

Since $V = E d$ we obtain

$$\frac{V_0}{K} = E d$$

$$E_0 \frac{V_0}{K d} = E \Rightarrow \boxed{E = \frac{E_0}{K}}$$

• What is the new capacitance

$$C = \frac{\text{charge}}{\text{voltage}}$$

$$= \frac{Q_0}{V_0/K} = K \frac{Q_0}{V_0}$$

$$\boxed{C = K C_0}$$

* Discussion of sample problem 26-5; page 602

$$= 13.5 \text{ pF} \quad \text{---} -Q$$

$$= 13.5 \times 10^{12} \text{ F} \quad \text{---} Q$$


$$V = 12.5 \text{ volts.}$$

$$U_i = \frac{1}{2} \frac{Q^2}{C} = 1100 \text{ pJ}$$

$$K = 6.5 \quad \text{---} \text{---} \text{---}$$

$$U_f = \frac{1}{2} \frac{Q^2}{K C} = 160 \text{ pJ}$$


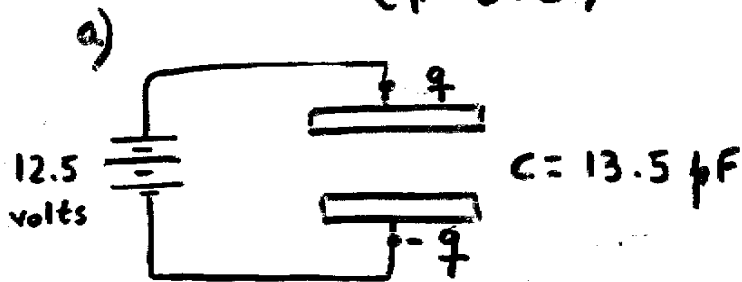
Example: Discussion of sample problem 26-5 ¹⁸
(p. 602)



A parallel-plate capacitor is initially connected to a battery

$$q = CV = 13.5 \times 10^{-12} \text{ F} \cdot 12.5 \text{ volts} = 1.68 \times 10^{-10} \text{ C}$$

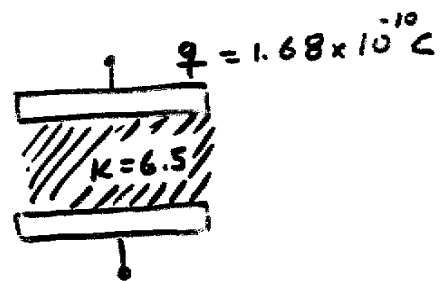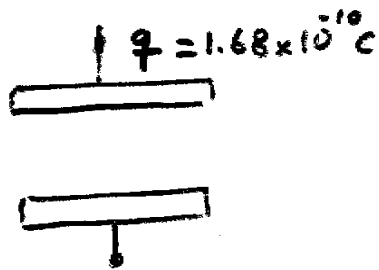b) The battery is disconnected and a dielectric ($\kappa = 6.5$) is slipped between the plates



What are the energies stored in the capacitor before and after introducing the dielectric?

BEFORE

$$U_i = \frac{1}{2} \frac{q^2}{C} = \frac{1}{2} \frac{(1.68 \times 10^{-10} \text{ C})^2}{13.5 \times 10^{-12} \text{ F}}$$


$$= 1055 \times 10^{-12} \text{ J}$$

AFTER

$$U_f = \frac{1}{2} \frac{q^2}{\kappa C}$$



$$= 162 \times 10^{-12} \text{ J}$$

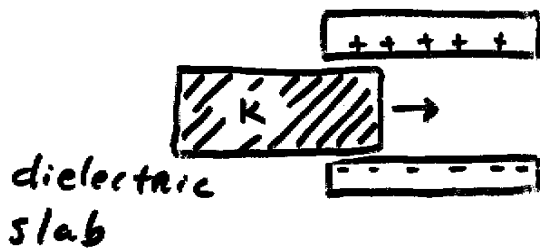Notice, the electrical energy decreases by a factor $K=6.5$ after the dielectric is introduced. 19



"the capacitor exerts a tiny tug on the slab"

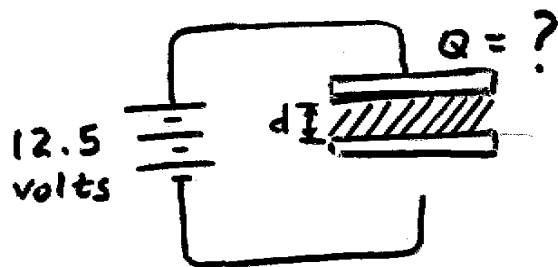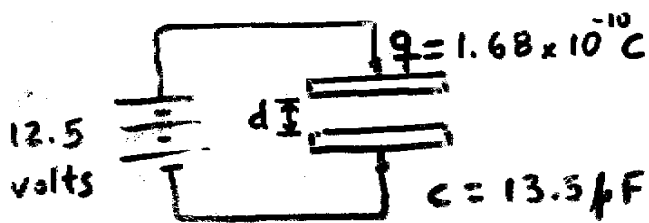Example: consider the previous problem but keeping the battery CONNECTED




Is $Q = q$


$Q < q$

$Q > q$

?

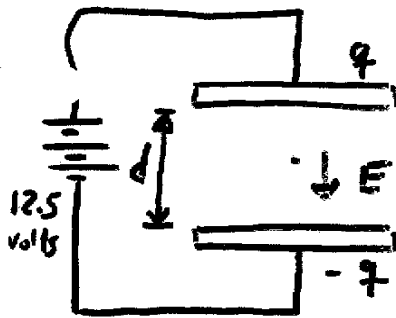

$$12.5 \text{ volts} = E d$$

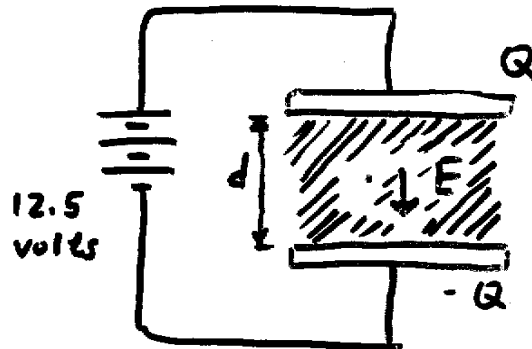

$$12.5 \text{ volts} = E d$$

So, the electric field has to be the same in both cases.

We also know a relationship between the electric field and the amount of charge in the plates

$$E = \frac{q/A}{\epsilon_0}$$


$$E = \frac{Q/A}{K \epsilon_0}$$

Therefore:



$$q = \frac{Q}{K}$$

$$\text{or } \boxed{Q = K q}$$



DIELECTRICS: a microscopic view

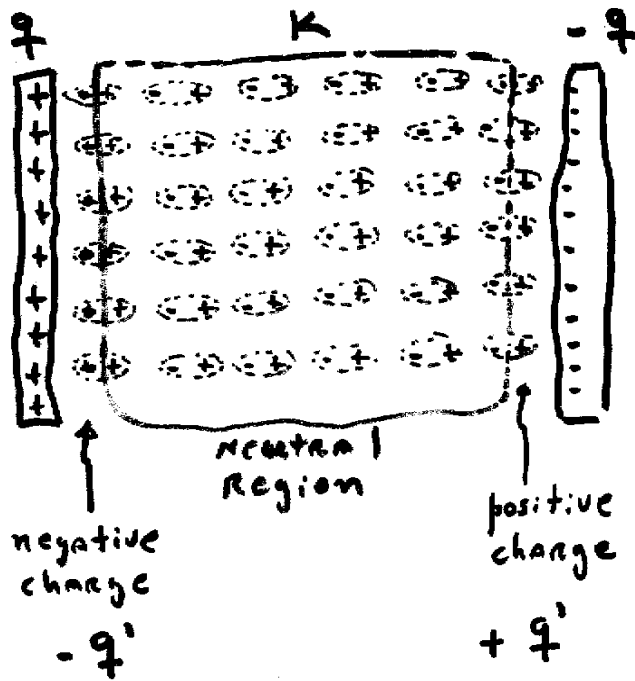

equivalent

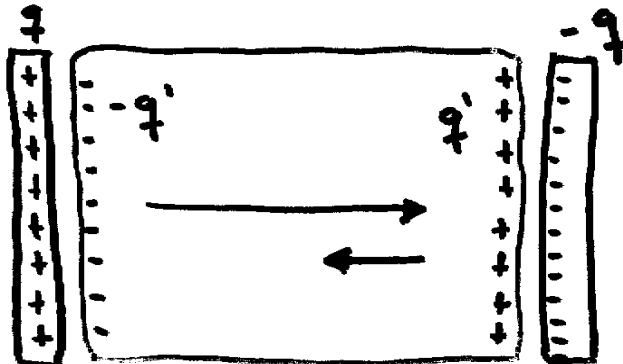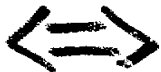

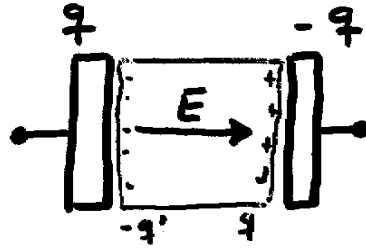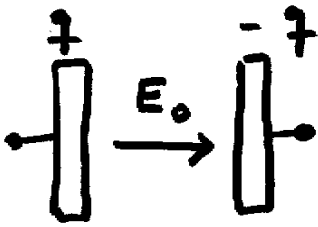
→ Electric field due to q and $-q$
 ← Electric field due to q' and $-q'$



$$\vec{E} = \vec{E}_0 + \vec{E}'$$

Let's use GAUSS' LAW

TO find q'

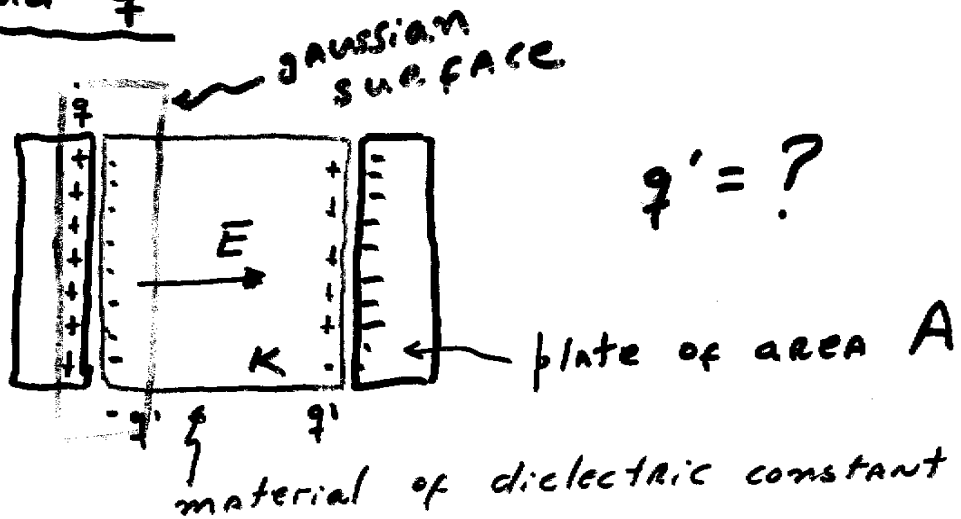

$$\epsilon_0 \int \vec{E} \cdot d\vec{s} = \text{charge inside} = q - q' \quad (1)$$

$$\epsilon_0 E A = q - q'$$

Electric
Field

$$\epsilon_0 \frac{E_0}{K} A = q - q' \quad (2)$$

But, let's remember that

$$E_0 = \frac{V}{\epsilon_0} = \frac{q}{A \epsilon_0}$$

(3)

value of the electric field without dielectric inside the plates.

So, replacing (3) in (2) we obtain

$$\frac{q}{k} = q - q'$$

(4)

Or

$$q' = \frac{k-1}{k} q$$

(5)

bound charge


free charge

Notice also that, replacing (4) in (1) we obtain

$$\int_S \epsilon_0 k E \cdot d\vec{S} = q$$


free charge only

GAUSS' LAW
WITH DIELECTRIC

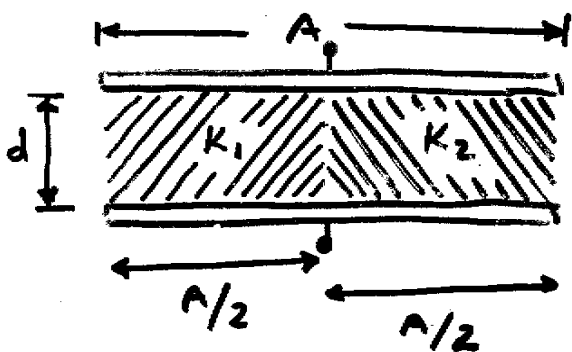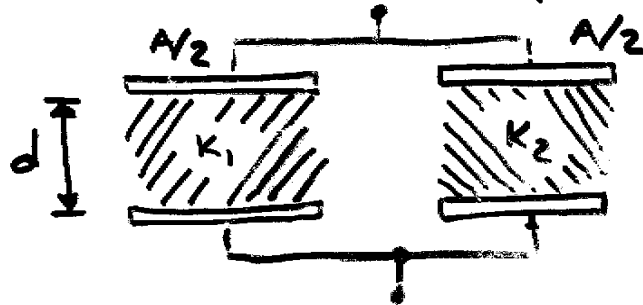Example

Parallel-plate capacitor
filled with 2 dielectrics
Find the capacitance
of the device.

Solution: The device looks like two capacitors
connected in parallel.




$$C_1 = K_1 \frac{(A/2) \epsilon_0}{d}$$

$$C_2 = K_2 \frac{(A/2) \epsilon_0}{d}$$

$$C = C_1 + C_2 \quad (\text{for parallel connection})$$

$$= \frac{(A/2) \epsilon_0}{d} (K_1 + K_2)$$

$$C = \frac{A \epsilon_0}{d} \cdot \frac{K_1 + K_2}{2}$$

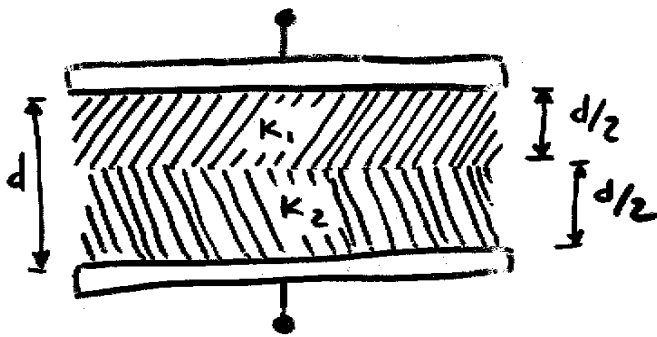
Example

Parallel-plate capacitors
filled with 2 dielectrics.

Find the capacitance
of the device

Solution: It is a little less obvious in this case ^{that} we have the equivalent of 2 capacitors connected in series.

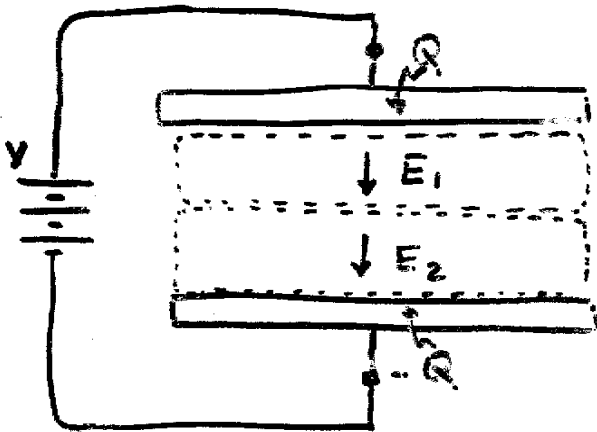So, let's follow a more secure method to solve this problem.




$$V = E_1 \cdot \frac{d}{2} + E_2 \cdot \frac{d}{2}$$

$$= \frac{E_0}{K_1} \cdot \frac{d}{2} + \frac{E_0}{K_2} \cdot \frac{d}{2}$$

$$= \frac{E_0 d}{2} \left(\frac{1}{K_1} + \frac{1}{K_2} \right)$$

$$\left(\text{but } E_0 = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0} \right)$$

$$= \frac{Qd}{A \epsilon_0 2} \left(\frac{1}{K_1} + \frac{1}{K_2} \right)$$
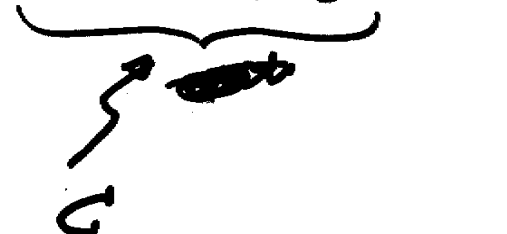
$$Q = \frac{A \epsilon_0}{d} \frac{2 K_1 K_2}{K_1 K_2} \quad \checkmark$$


The diagram shows a handwritten bracket under the fraction $\frac{A \epsilon_0}{d} \frac{2 K_1 K_2}{K_1 K_2}$. An arrow points from the bracket to a scribbled-out area. A checkmark is drawn to the right of the equation.

Example Find the charge distribution in the plates.


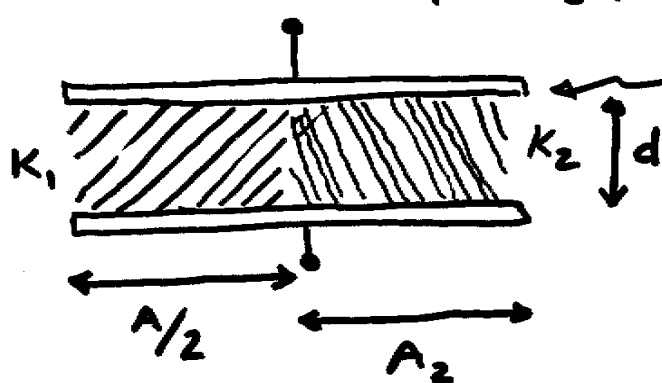



plate of area A

Find the capacitance.

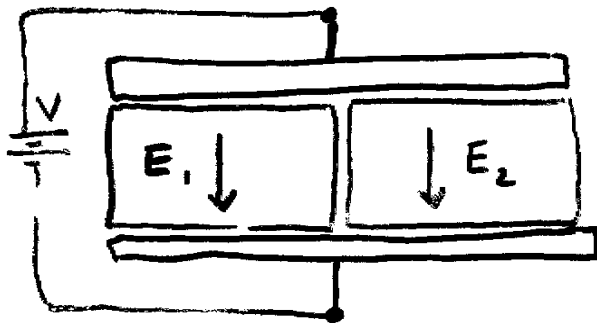

$$\left. \begin{array}{l} V = E_1 d \\ V = E_2 d \end{array} \right\} \Rightarrow E_1 = E_2$$

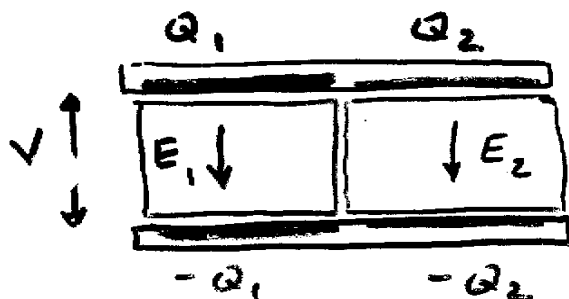Since $K_1 \neq K_2$ and $E_1 = E_2$ then we suspect that the charge distribution is not uniform over the plates




What is the relationship between the charges?


$$E_1 = \frac{\text{Field without dielectric}}{K_1} = \frac{\frac{Q_1}{(A/2)\epsilon_0}}{K_1} = \frac{2Q_1}{A\epsilon_0 K_1}$$

$$E_2 = \frac{\text{field without dielectric}}{K_2} = \frac{2Q_2}{A\epsilon_0 K_2}$$
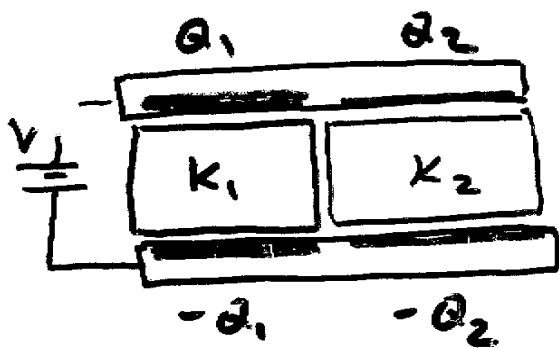
$$E_1 = E_2 \Rightarrow \frac{Q_1}{K_1} = \frac{Q_2}{K_2} \quad (1)$$



Equivalent
to

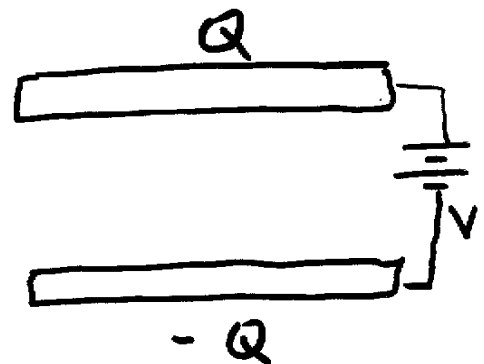

$$Q = C V$$

$$Q = (Q_1 + Q_2) = Q_1 + \frac{K_2}{K_1} Q_1$$

$$= Q_1 \left(1 + \frac{K_2}{K_1} \right)$$

(2)

But $Q_1 = C_1 V$ where $C_1 = \frac{(A/2) \epsilon_0}{d} k_1$ ²⁹

$$Q_1 = \frac{A \epsilon_0 k_1 V}{2d} \quad (3)$$



So, replacing (3) in (2) we obtain

$$Q = \underbrace{\frac{A \epsilon_0 k_1}{2d} \left(1 + \frac{k_2}{k_1}\right)} V$$


$$C = \frac{A \epsilon_0}{2d} (k_1 + k_2)$$

Ground: A very large conductor that can supply an unlimited amount of charge

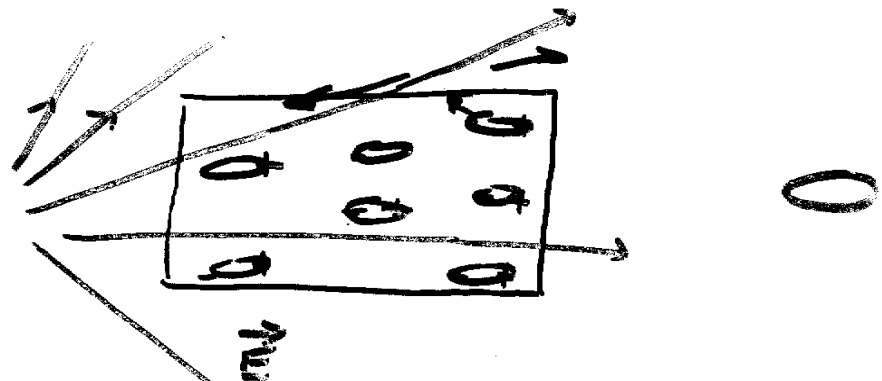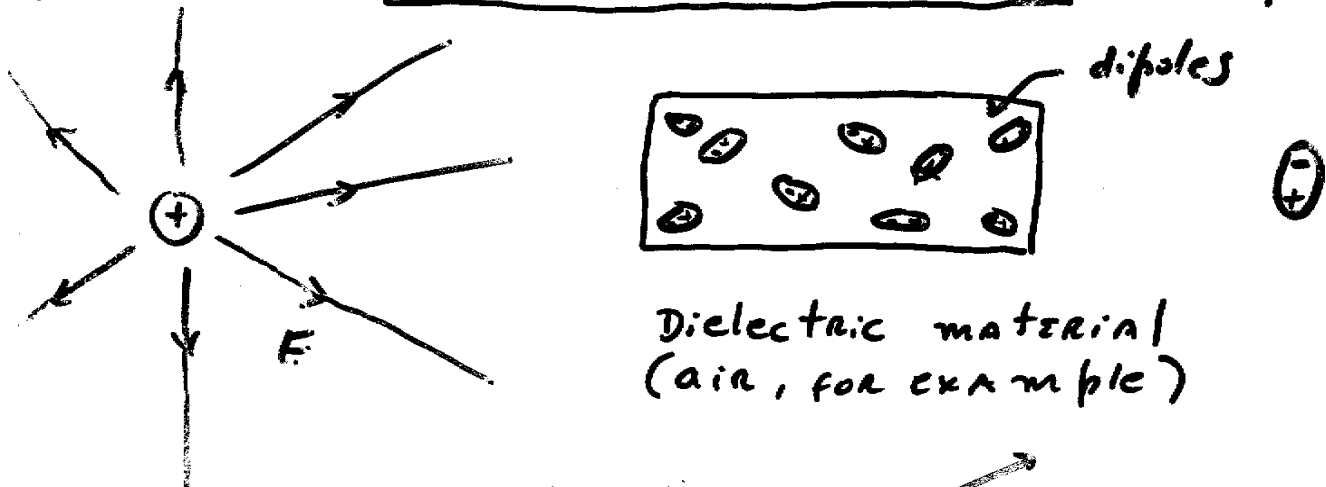Review on Dielectric Breakdown: sample problem 23-6, p. 565



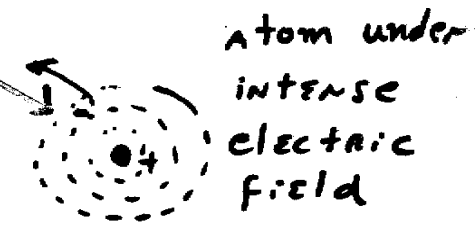Many nonconducting materials become ionized in very high electric fields \vec{E} . This phenomenon is called Dielectric Breakdown.



Atom under intense electric field


Reading assignment:

- Ink-Jet Printing, page 533
- sample problem 23-8, page 568
- ! - what is "electrical breakdown", read sample - problem 23-6, page 565
- ! - Problem 37 P

PRACTICE PROBLEMS

① = H-22 QUESTION #3 (p. 517) Ans. a) & b)

② Sample problem 22-2 (p. 512)

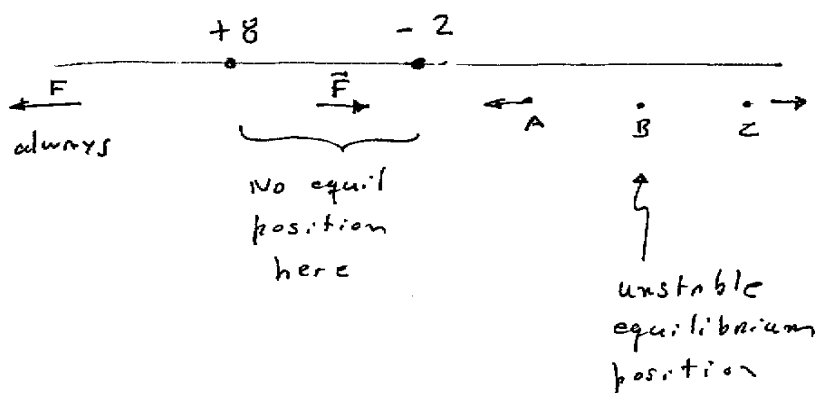


③ Sample problem 22-1 (p. 511)

Part b) Highlight that ~~eventhough~~ particle 3 is in between, still

$$F_{12} = \frac{1}{4\pi\epsilon_0} \frac{q_1 q_2}{r_{12}^2}$$

④ Sample problem 23-3 (p. 529)

Problem 23P (Chapter - 23)

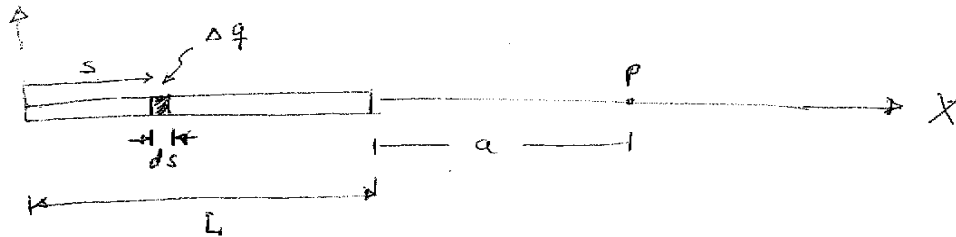

$$a) \quad \Delta q = \left(-\frac{q}{L}\right) \Delta s$$

$$b) \quad \Delta E = \frac{1}{4\pi\epsilon_0} \frac{(\Delta q)}{(L+a-s)^2} = \frac{1}{4\pi\epsilon_0} \frac{\left(-\frac{q}{L}\right) \Delta s}{(L+a-s)^2}$$

$$E = -\frac{1}{4\pi\epsilon_0} \frac{q}{L} \int_0^L \frac{ds}{(L+a-s)^2} = -\frac{1}{4\pi\epsilon_0} \frac{q}{L} \frac{1}{(L+a-s)} \Big|_0^L$$

notice


$$\frac{d}{ds} \left\{ \frac{1}{(L+a-s)} \right\} = (-1) \frac{1}{(L+a-s)^2} (-1) = \frac{1}{(L+a-s)^2}$$

$$= -\frac{1}{4\pi\epsilon_0} \frac{q}{L} \left[\frac{1}{a} - \frac{1}{L+a} \right] = -\frac{q}{4\pi\epsilon_0} \frac{1}{a(L+a)}$$

$$c) \quad E = -\frac{q}{4\pi\epsilon_0} \frac{1}{a(L+a)} \xrightarrow{a \rightarrow \infty} -\frac{q}{4\pi\epsilon_0} \frac{1}{a^2} \quad \checkmark$$

Problem #25 CH-23

$$\Delta q = \lambda ds$$

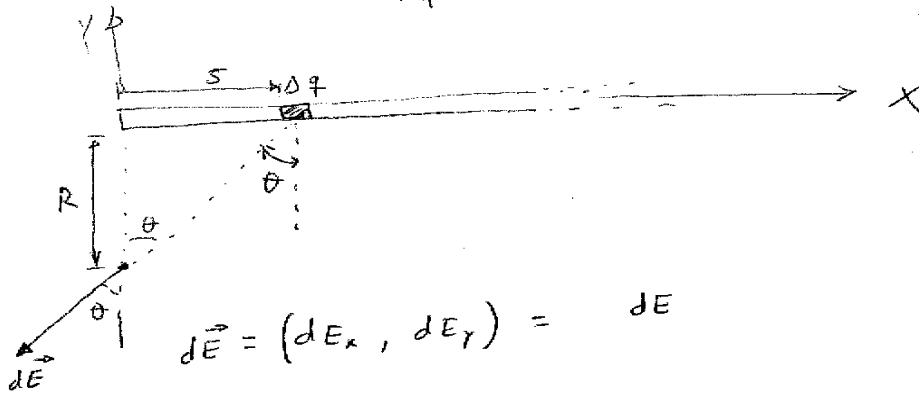

$$d\vec{E} = (dE_x, dE_y) = dE$$

$$dE_x = -dE \sin \theta = -\left(\frac{1}{4\pi\epsilon_0} \frac{\Delta q}{r^2 + s^2}\right) \frac{s}{(r^2 + s^2)^{1/2}}$$

$$E_x = -\frac{1}{4\pi\epsilon_0} \int \frac{(\Delta q) s}{(r^2 + s^2)^{3/2}} = -\frac{\lambda}{4\pi\epsilon_0} \int_0^{\infty} \frac{s ds}{(r^2 + s^2)^{3/2}}$$

$$\text{Notice: } \frac{d}{ds} \left(\frac{-1}{(r^2 + s^2)^{1/2}} \right) = -1 \left(-\frac{1}{2} \right) (r^2 + s^2)^{-3/2} 2s$$

$$= \frac{s}{(r^2 + s^2)^{3/2}}$$

$$E_x = + \frac{\lambda}{4\pi\epsilon_0} \frac{1}{(r^2 + s^2)^{1/2}} \Big|_0^{\infty} = \boxed{-\frac{\lambda}{4\pi\epsilon_0} \frac{1}{R} = E_x}$$

$$dE_y = -dE \cos \theta = -\left(\frac{1}{4\pi\epsilon_0} \frac{\Delta q}{r^2 + s^2}\right) \frac{R}{(r^2 + s^2)^{1/2}}$$


$$E_y = -\frac{1}{4\pi\epsilon_0} R \lambda \int \frac{ds}{(r^2 + s^2)^{3/2}} = -\frac{1}{4\pi\epsilon_0} R \lambda \frac{s}{(r^2 + s^2)^{1/2} R^2} \Big|_0^{\infty}$$

$$= \frac{-\lambda}{4\pi\epsilon_0 R} (1 - 0)$$

$$\boxed{E_y = \frac{-\lambda}{4\pi\epsilon_0 R}}$$

Problem 46P CH-24

a)

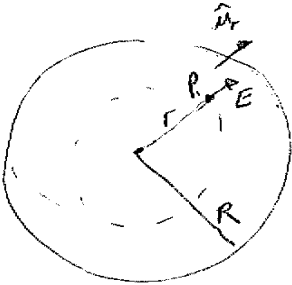

$$E \times \pi r^2 = \int \frac{\rho}{3} \pi r^3 / \epsilon_0$$

$$E = \frac{\rho}{3\epsilon_0} r$$


$$\vec{E} = \frac{\rho}{3\epsilon_0} r \hat{u}_r$$

\Leftrightarrow

$$\vec{E} = \frac{\rho}{3\epsilon_0} \vec{r}$$


It does not depend on R

b)

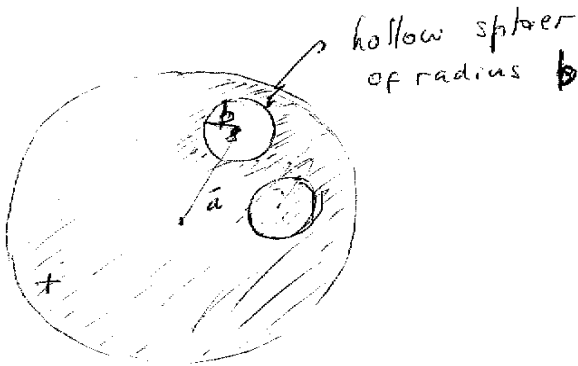


hollow sphere of radius b

\Leftrightarrow

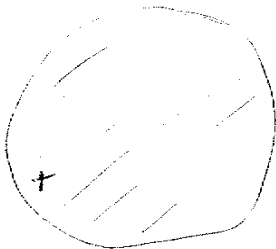

+

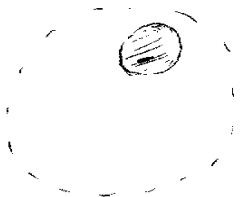


$$\vec{E}(\text{at } P) = \vec{E}_{\text{due to the big sphere (positively charged)}} + \vec{E}_{\text{due to the small sphere (negatively charged)}}$$

$$= \frac{\rho}{3\epsilon_0} (\vec{a} + \vec{r}) + \frac{(-\rho)}{3\epsilon_0} \vec{r}$$


$$\vec{E}(\text{at } P) = \frac{\rho}{3\epsilon_0} \vec{a}$$



Problem # 28E CH-24

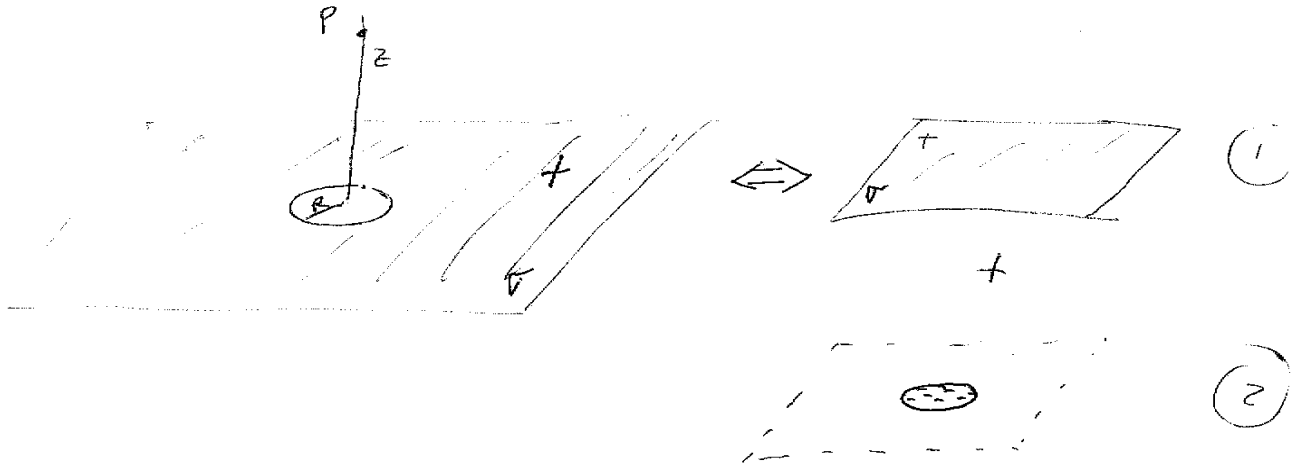




So,

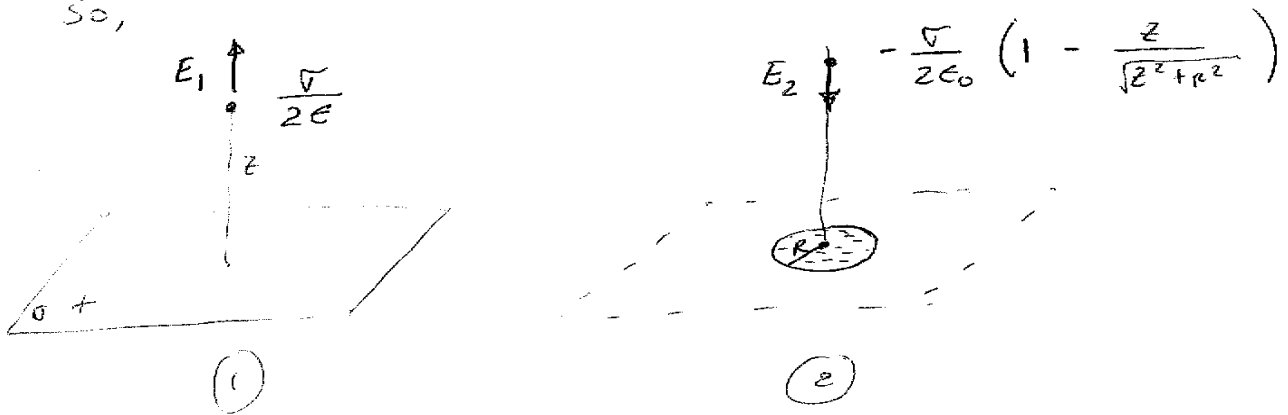

$$E(z) = \frac{\sigma}{2\epsilon_0} - \frac{\sigma}{2\epsilon_0} \left(1 - \frac{z}{\sqrt{z^2 + R^2}} \right) = \frac{\sigma}{2\epsilon_0} \frac{z}{\sqrt{z^2 + R^2}}$$

PRACTICE PROBLEMS

checkpoint #6, page 578

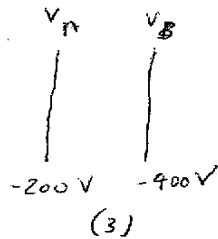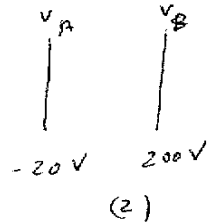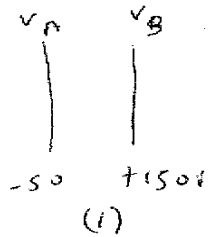

$$E = -\frac{\Delta V}{\Delta x} = -\frac{V_B - V_A}{d}$$


$$\frac{200V}{d}$$

$$\frac{220}{d}$$

$$\frac{200}{d}$$

$\leftarrow F$

sample problem 25-5

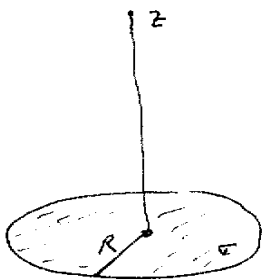

$$V(0,0,z) = \frac{\sigma}{2\epsilon_0} \left(\sqrt{z^2 + R^2} - z \right)$$

$$E_z = -\frac{\partial V}{\partial z} = -\frac{\sigma}{2\epsilon_0} \left(\frac{z}{\sqrt{z^2 + R^2}} - 1 \right)$$

$$= \frac{\sigma}{2\epsilon_0} \left(1 - \frac{z}{\sqrt{z^2 + R^2}} \right)$$