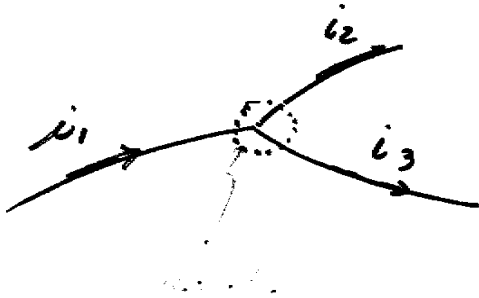



Lecture

STEADY CURRENTS OF
CONDUCTION ELECTRONS MOVING
through metallic conductors




CHARGE CONSERVATION
 IMPLIES:

$$i_1 = i_2 + i_3$$

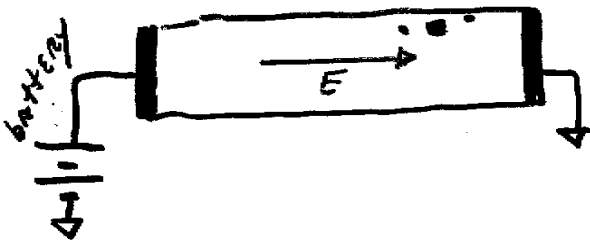



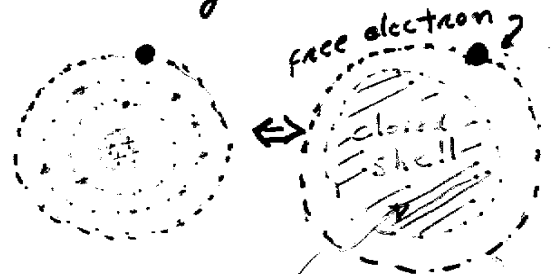
Electric fields \vec{E} act
inside the material,
 EXERTING FORCES ON THE
 CONDUCTION ELECTRONS,
 CAUSING THEM TO MOVE, AND
 THUS ESTABLISHING A CURRENT



electrons in the
 closed shell do not
 participate in the
 +

• free electrons

wire E →

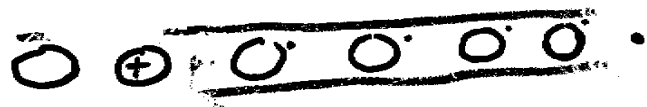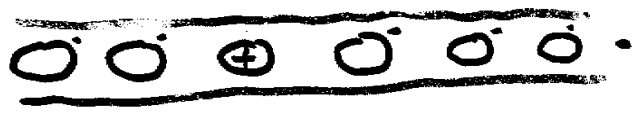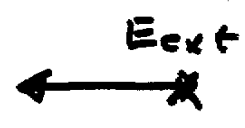


negative charges


positive charges

⇔ equivalent

Definition of CURRENT

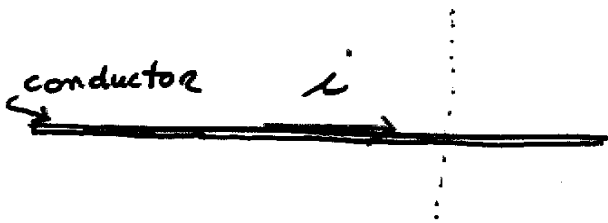

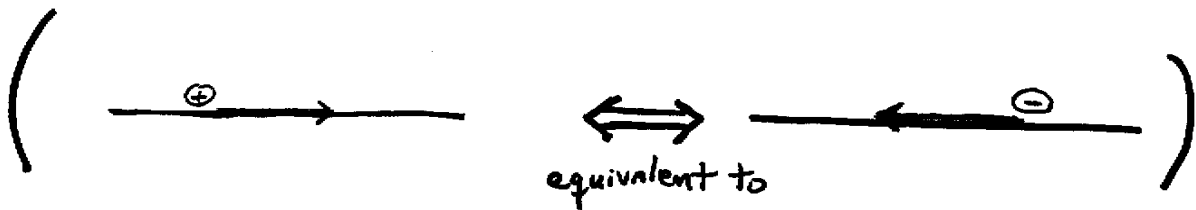
current arrow drawn in the direction in which positive charge carrier would move.



$$i = \frac{dq}{dt}$$

unit of i : ampere


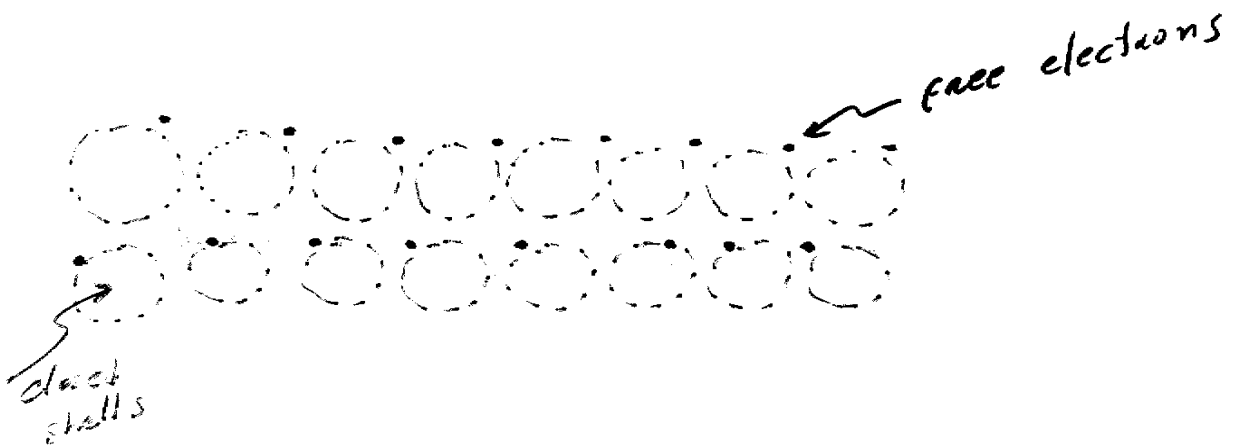
$$\text{ampere} = \frac{\text{coulomb}}{\text{sec}}$$




Each atom contributes with 1 free electron Cu, Au
 2 " " " Zn, Cd

Current Density. - \vec{j}

5

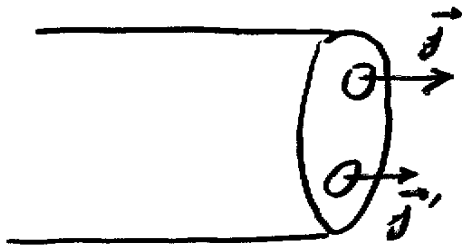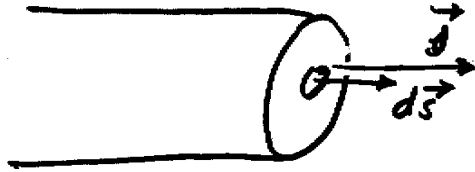

$$i = \int \vec{j} \cdot d\vec{S}$$

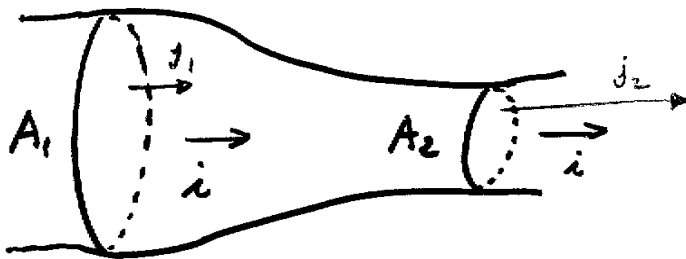


$$j_1 = \frac{i}{A_1}$$

$$j_2 = \frac{i}{A_2}$$


DRIFT SPEED

Comparison

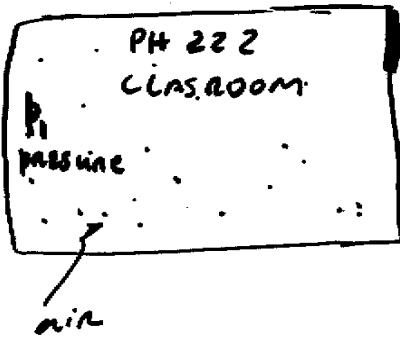


each molecule moves
at ~ 400 m/s
But, AVERAGE velocity
 $\langle v \rangle = 0$

under a pressure
difference $p_2 - p_1$

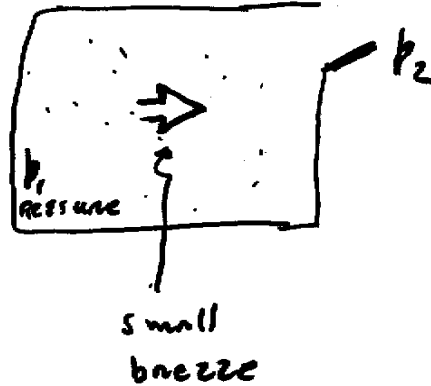


$\langle v \rangle \neq 0$
air molecules acquire
a small drift velocity,
superimposed to their
400 m/s instantaneous
speed.

chunk of metal

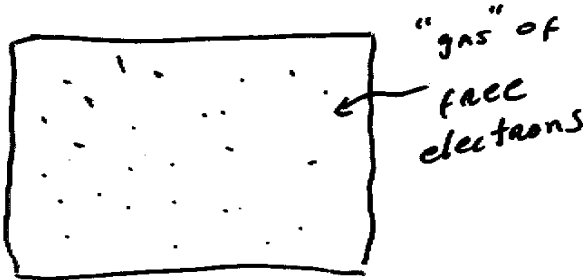

At room temperature, electrons move
with speed $\sim 10^7$ m/s
But $\langle v \rangle = 0$ (Because e^- move
randomly)

under an electric
field E

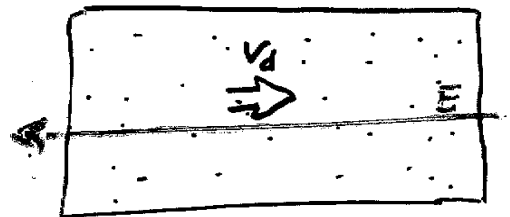

the free electrons acquire
a drift speed v_D
 $v_D \approx 5 \times 10^{-7}$ m/s

Evaluating the drift speed v_d

7



Copper

$$\blacksquare M = 63.5 \text{ gr/mol}$$

$$1 \text{ mol of } \text{Cu} \text{ atoms} \text{ --- } 63.5 \text{ gr}$$

$$6.023 \times 10^{23} \text{ atoms of Cu --- } 63.5 \text{ gr}$$

$$\blacksquare \text{ density} = 8.93 \text{ gr/cm}^3$$

$$6.023 \times 10^{23} \text{ atoms of Cu --- } 63.5 \text{ gr}$$

$$x = \# \text{ of atoms in } 1 \text{ cm}^3 \text{ --- } 8.93 \text{ gr}$$

$$\frac{8.93}{63.5} \times 6.023 \times 10^{23} \text{ atoms/cm}^3$$


$$\blacksquare 1 \text{ free electron per atom}$$

$$\Rightarrow \frac{8.93}{63.5} \times 6.023 \times 10^{23} \text{ free-electrons/cm}^3$$

$$= n \text{ number of carriers per unit volume}$$

$$= 8.5 \times 10^{22} \text{ free-electrons/cm}^3$$

$$= 8.5 \times 10^{28} \text{ /m}^3$$

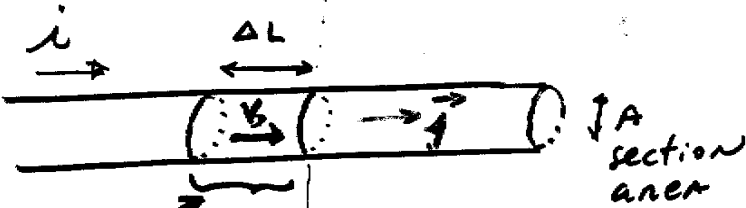

$$e = 1.6 \times 10^{-19} \text{ C}$$

electron charge

Amount of charge Δq in this volume $\Delta q = n e \times \text{volume}$

$$= n e \times \Delta L \times A = \Delta q$$

All this charge will cross the plane PP' in a time Δt


$$\Delta t = \frac{\Delta L}{v_d}$$

$$i = \frac{\Delta q}{\Delta t} = n e v_d A$$

velocity of the carriers
amount of charge in each carrier
of carriers per volume

$$j = \frac{i}{A} = n e v_d$$

$$j = n e v_d$$

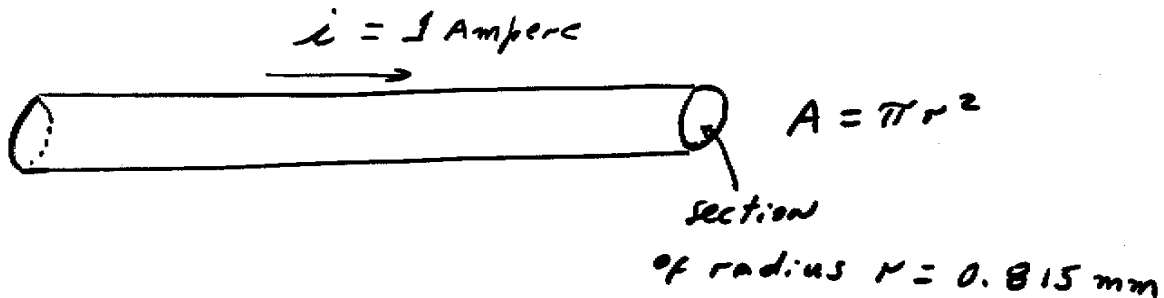

$$j = ne v_D$$

$$\frac{i}{A} = ne v_D \Rightarrow \boxed{\frac{i}{neA} = v_D}$$

$$\frac{1 \text{ C/s}}{(8.5 \times 10^{28} / \text{m}^3)(1.6 \times 10^{-19} \text{ C}) \pi (0.8 \times 10^{-3} \text{ m})^2} = v_D$$


$$3.5 \times 10^{-5} \text{ m/s} = v_D$$

Exercise

From Paul A. Tipler; "Physics"; vol-2; 4th Ed.
 How long would it take for an electron
 to drift from your car battery to the
 starter motor, a distance of about
 1 m, if its drift speed is $3.5 \times 10^{-5} \text{ m/s}$? Answer:
 ~ 8 hours

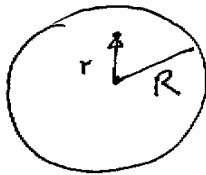Example (similar to Problem 10 CH-27)

A cylinder carries a current, which is established by a current density $j = j(r)$.



Consider the following current densities:

a) $j(r) = j_0$

b) $j(r) = j_0 \frac{r}{R}$

c) $j(r) = j_0 \left(1 - \frac{r}{R}\right)$

Calculate the total current flowing through the cylinder

Solution

a) $I = j_0 \times \text{area} = \boxed{j_0 \times \pi R^2 = I}$

b)

Diagram for part b: A circular cross-section with a differential area element $dA = 2\pi r dr$ shown as a shaded ring. Below it is a graph of current density j versus radius r , showing a linear relationship $j = j_0 \frac{r}{R}$.

$$dA = 2\pi r dr$$

$$dI = j dA = j_0 \frac{r}{R} 2\pi r dr$$

$$\int dI = \int_0^R \left(j_0 \frac{r}{R}\right) 2\pi r dr = j_0 \frac{2\pi}{R} \int_0^R r^2 dr = j_0 \frac{2\pi}{R} \frac{R^3}{3}$$

$$\boxed{I = \frac{2}{3} j_0 \pi R^2}$$

c)

Diagram for part c: A circular cross-section with a differential area element $dA = 2\pi r dr$ shown as a shaded ring. Below it is a graph of current density j versus radius r , showing a linear relationship $j = j_0 \left(1 - \frac{r}{R}\right)$.

$$dI = j dA = j_0 \left(1 - \frac{r}{R}\right) 2\pi r dr$$

$$I = \int dI = \int_0^R j_0 \left(1 - \frac{r}{R}\right) 2\pi r dr$$

$$= j_0 2\pi \frac{R^2}{2} - j_0 \frac{2\pi}{R} \frac{R^3}{3} =$$

$$= j_0 \pi R^2 - j_0 \frac{2}{3} \pi R^2 \Rightarrow \boxed{I = \frac{1}{3} \pi R^2}$$


RESISTANCE and RESISTIVITY

R

MACROSCOPIC
object PROPERTY

ρ


material
property

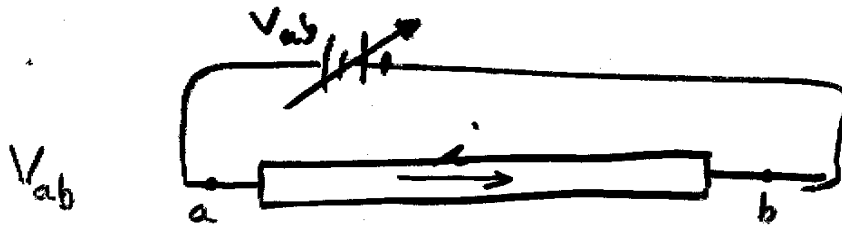


$$R = \frac{V_{ab}}{i}$$

units:
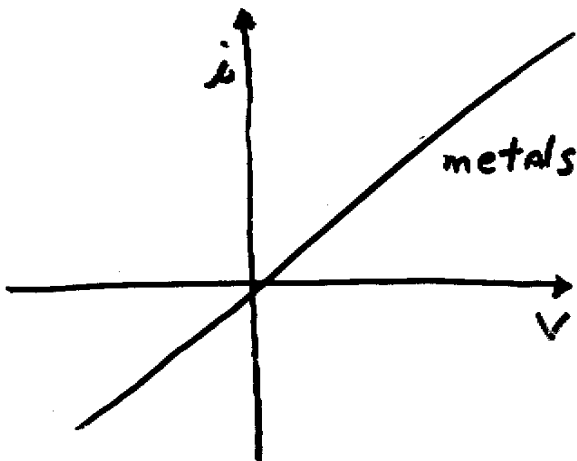
$$\text{ohm} = \frac{\text{volt}}{\text{Amp}}$$




Some materials
obey Ohm's "law"

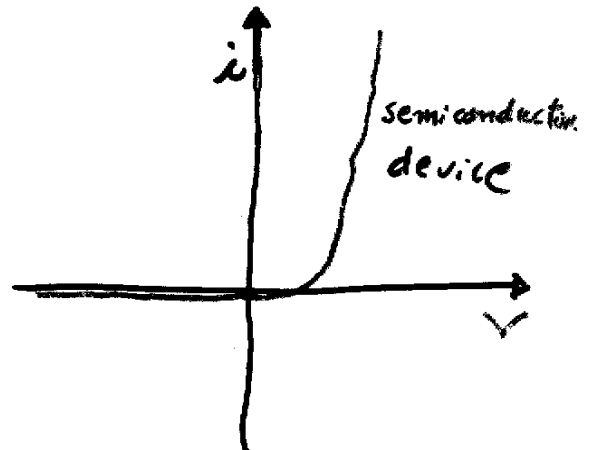


other materials
do not follow
Ohm's "law"

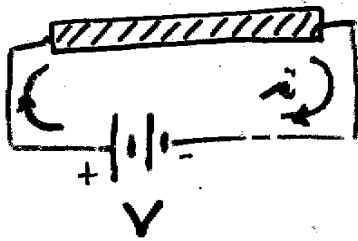Material that is said to obey "ohm's law" 12




V	i	$R = \frac{V}{i}$
1V	0.2A	
2V	0.4A	
3	0.6A	

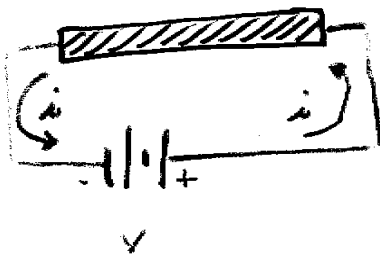




V	i	$R = \frac{V}{i}$
1.5V	0.3A	
2.5V	0.5A	
3.5V	0.7A	


if all these number turn out to be the same, then we say that the material is ohmic

V	i	R
3V	0.6A	
2V	0.4A	
1V	0.2A	
-1.5	-0.3	

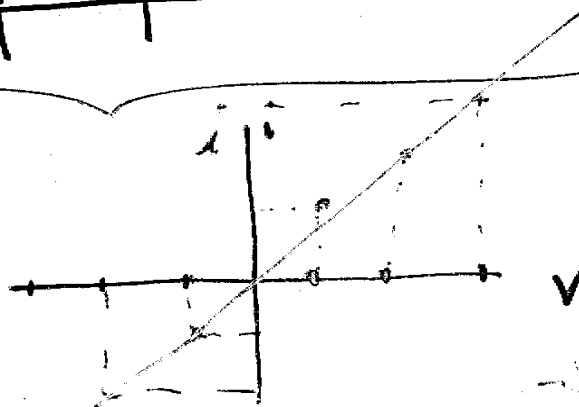

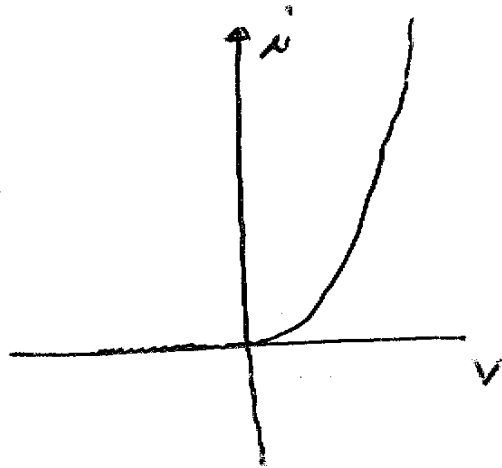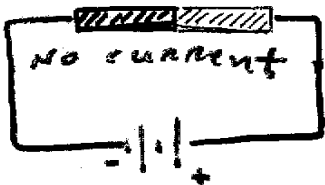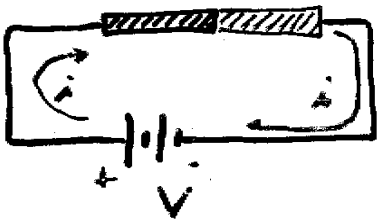A diode, composed of 2 different semiconductor materials, DOES NOT obey ohm's law



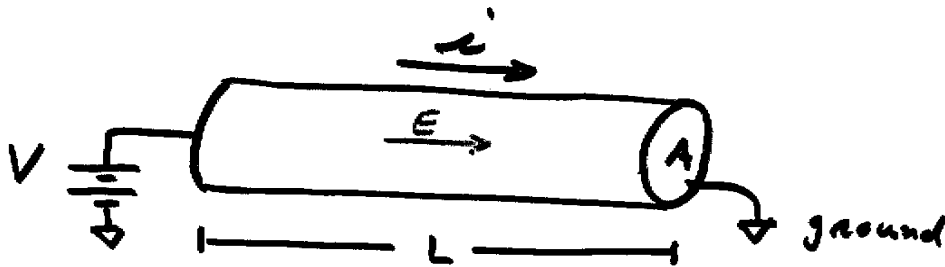

$$V = EL$$

$$= \rho j L$$


$$= \rho \frac{i}{A} L \Rightarrow V = \underbrace{\rho L}_{R} \frac{i}{A}$$

$$\frac{V}{i} = \boxed{R = \rho \frac{L}{A}}$$

RESISTANCE material property geometry

units of ρ : ohm-meter
= $\Omega \cdot m$

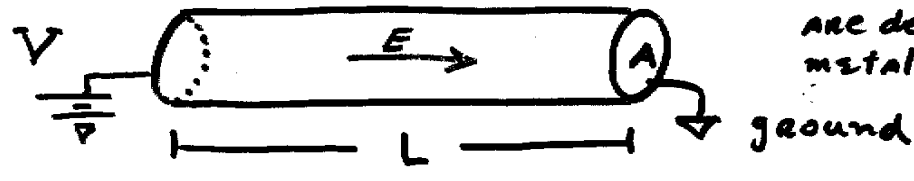RESISTIVITY (ρ), CONDUCTIVITY (σ), ELECTRIC FIELD (E), RESISTANCE (R)



The following analysis is valid whether we are dealing with a metal or a homogeneous semiconductor material

The higher $V \rightarrow$ the higher \vec{E} (electric field)

the higher $\vec{E} \rightarrow$ the higher \vec{j} (current density)

$$\vec{j} = \sigma \vec{E}$$

↑
conductivity

Definition of resistivity ρ

$$\rho = \frac{1}{\sigma}$$

$$\vec{j} = \frac{1}{\rho} \vec{E}$$

RESISTIVITY

SILVER $1.62 \times 10^{-8} \Omega\text{-m}$

ALUMINUM $2.75 \times 10^{-8} \Omega\text{-m}$

METALS

SILICON (pure) $2.5 \times 10^3 \Omega\text{-m}$

SILICON (n type) $8.7 \times 10^{-4} \Omega\text{-m}$

(silicon + phosphorous
impurities)

SILICON (p-type) $2.8 \times 10^{-3} \Omega\text{-m}$

(silicon + Aluminum
impurities)


SEMI-CONDUCTORS

GLASS $10^{10} - 10^{14} \Omega\text{-m}$

Fused quartz $10^{16} \Omega\text{-m}$

INSULATORS

Microscopic view

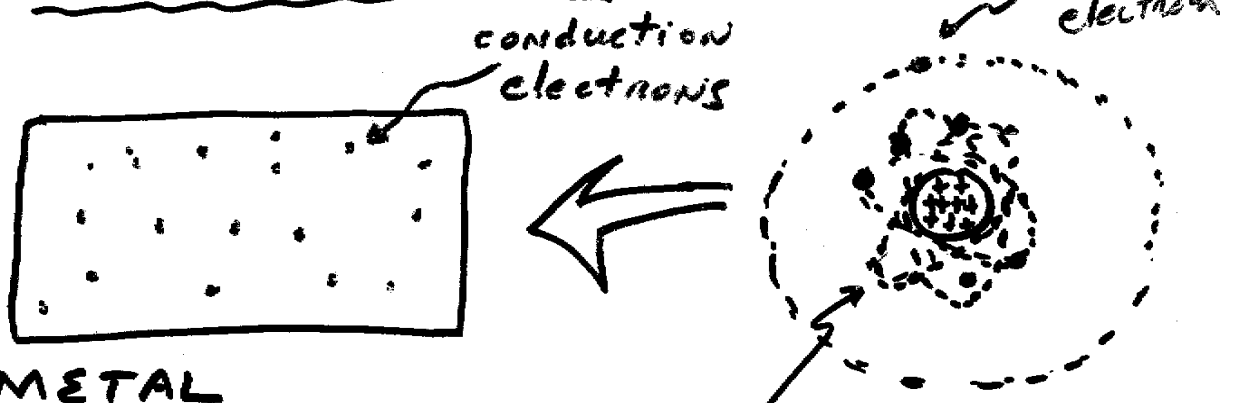

METAL


"Free-electron model"


This model assumes that electrons collide not with one another (!) but only with atoms of the metal

CASE OF:

1 free-electron per atom

electrons tight to the atom

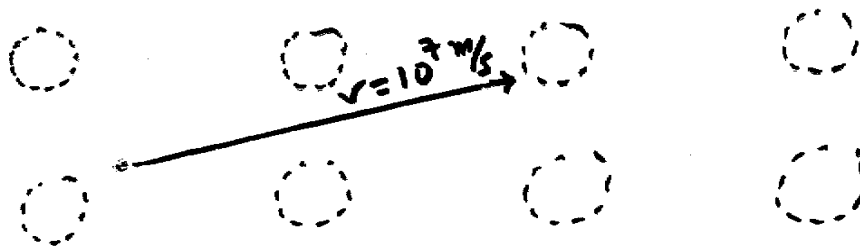

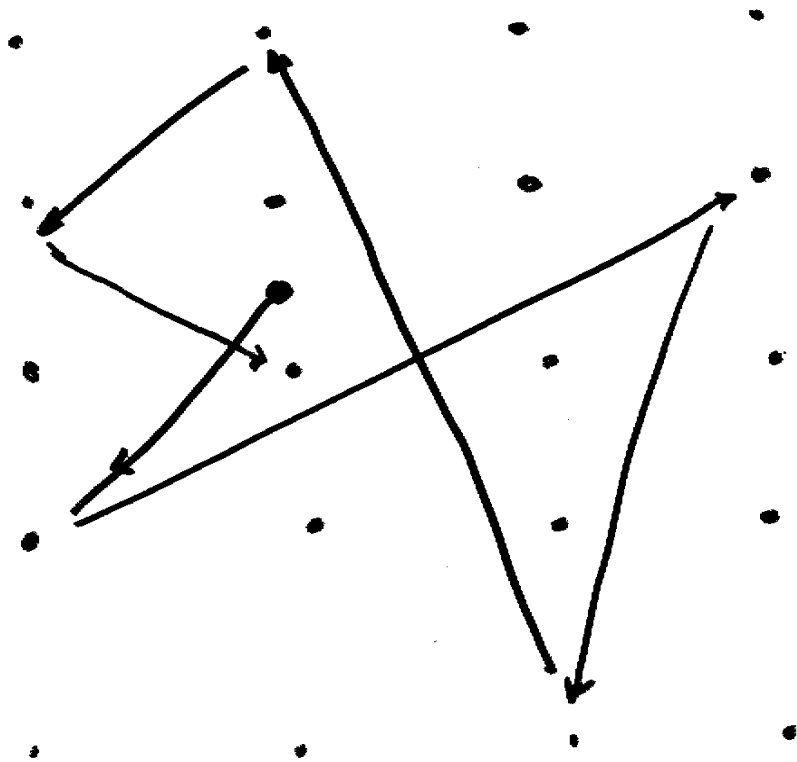

In average, the free electrons do not have a net displacement

$$a = \frac{F}{m} = \frac{eE}{m}$$

$$\langle v \rangle = \langle a \tau \rangle = \frac{eE}{m} \tau \quad (1)$$

$$j = ne \langle v \rangle$$

$$\langle v \rangle = \frac{eE}{m} \tau = \frac{j}{ne}$$

$$\left(\frac{e^2 n \tau}{m} \right) E = j$$

$$\sigma = \frac{e^2 n \tau}{m}$$

$$\rho = \frac{m}{e^2 n \tau}$$

Sample Problem 27-5

Specially read part (b) of this sample problem

Additional advanced reading.

N. Ashcroft and N. Mermin; "SOLID STATE PHYSICS"; saunders College Ed.


- page 1 to 10
- Last paragraph on page 215, and page 216

"the conductivity of a perfect
periodic crystal is infinite"

"metals have an electrical resistance
because no real solid is a perfect

crystal: missing atoms
dislocations
impurities
thermal vibration



CIRCUITS

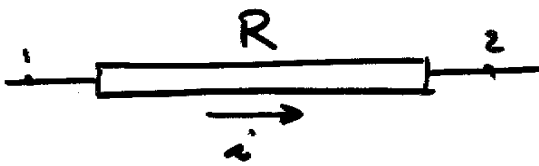


$$V_{12} = R i$$

Symbol 

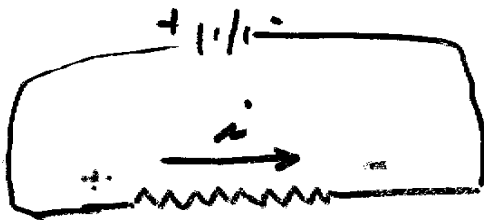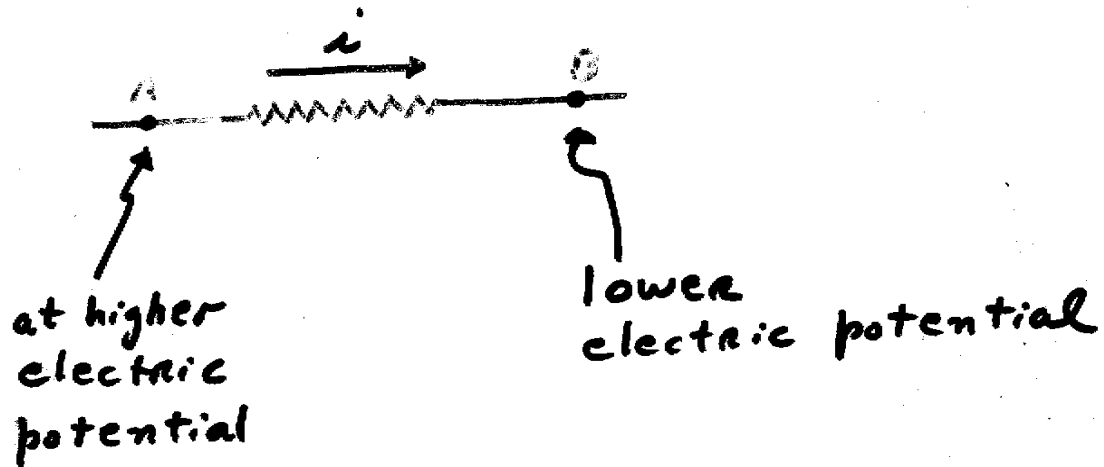Unit of R $\frac{\text{volt}}{\text{Amp}} = \text{ohm}$



SINGLE-LOOP circuits

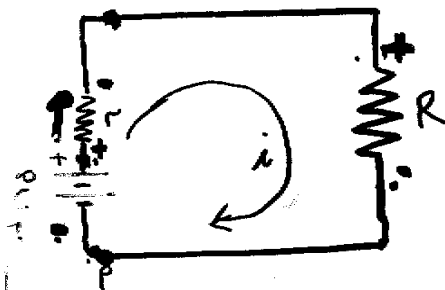

$$\cancel{\frac{1}{r}} + \mathcal{E} - ri - Ri = \cancel{\frac{1}{r}}$$

$$\mathcal{E} = (r + R)i$$

$$i = \frac{\mathcal{E}}{r + R}$$

Energy source { battery
electric generator
solar cell!

\mathcal{E} is called "electromotive force"

outdated phrase


\mathcal{E} is not a force

Unit of \mathcal{E} is volts!

Resistors connected in series

$$V_{ac} = V_{ab} + V_{bc}$$

$$= R_1 i + R_2 i$$

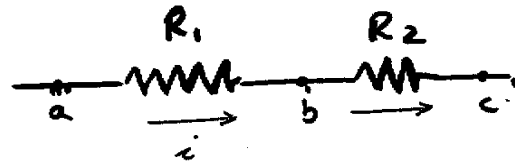

$= \underbrace{(R_1 + R_2)} i$ ← This expression tells us that the resistors arrangement above shown

$$V_{ac} = R_{eq} i$$

is equivalent to



provided that

$$R_{equiv} = R_1 + R_2$$


For many resistances connected in series

$$R_{equiv} = R_1 + R_2 + R_3 + \dots$$

Resistors connected in PARALLEL

$$V_{ab} = R_1 i_1$$

$$V_{ab} = R_2 i_2$$

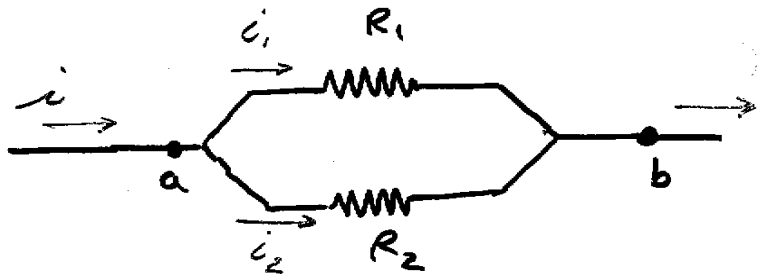

$$i = i_1 + i_2$$

$$= \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2}$$

$$i = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_{ab}$$

This expression tells us that the resistors arrangement shown above is equivalent to

$$i \left(\frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right)} \right) = V_{ab}$$




$$i R_{eq} = V_{ab}$$

if

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \longrightarrow \frac{1}{R_{equiv}} = \frac{1}{R_1} + \frac{1}{R_2}$$


For many resistors connected in parallel

$$\frac{1}{R_{equiv}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

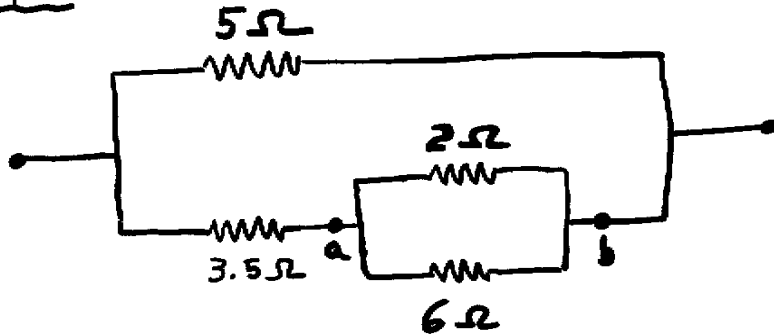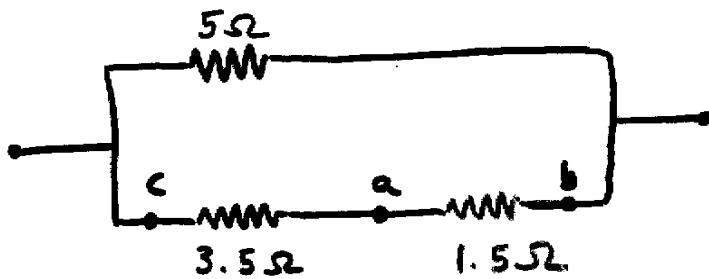Example


ab
PARALLEL CONNECTION

$$\frac{1}{R_{eq}} = \frac{1}{2\Omega} + \frac{1}{6\Omega} = \frac{4}{6\Omega} \Rightarrow R_{eq} = 1.5\Omega$$




cb
SERIES CONNECTION
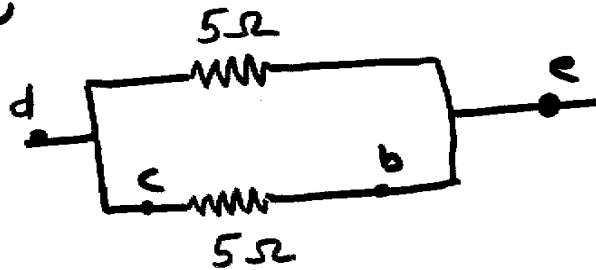
$$R_{eq} = 1.5\Omega + 3.5\Omega = 5\Omega$$




de
parallel connection

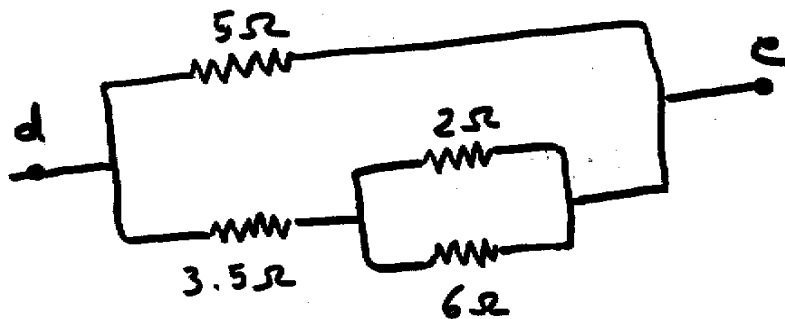
$$\frac{1}{R_{eq}} = \frac{1}{5\Omega} + \frac{1}{5\Omega} = \frac{2}{5\Omega} \Rightarrow R_{eq} = 2.5\Omega$$



this circuit is equivalent to

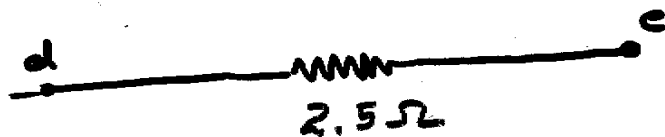

Multiloop circuit

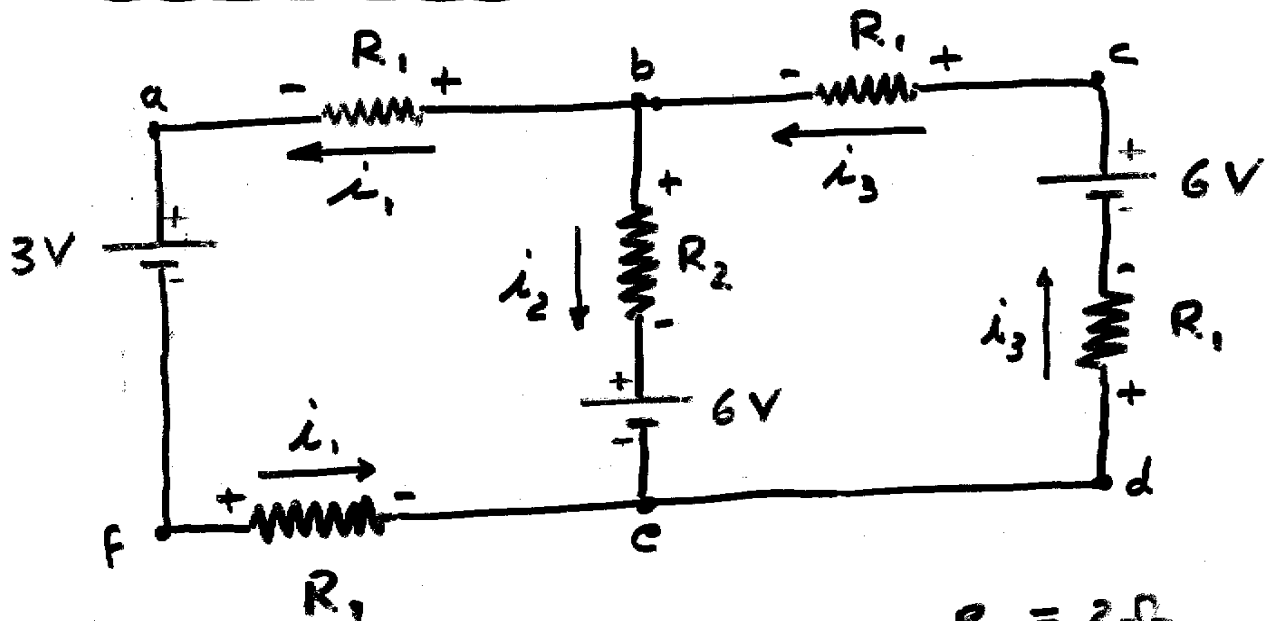

UNKNOWN : i_1, i_2, i_3

$$R_1 = 2\Omega$$

$$R_2 = 4\Omega$$

Loop bedc

$$\cancel{0} - i_2 R_2 - 6V - i_3 R_1 + 6V - i_3 R_1 = \cancel{0}$$

$$\Rightarrow \boxed{-i_2 R_2 - 2i_3 R_1 = 0} \quad (1)$$

Loop befa

$$\cancel{0} - i_2 R_2 - 6V + i_1 R_1 + 3V + i_1 R_1 = \cancel{0}$$

$$\Rightarrow \boxed{-i_2 R_2 + 2i_1 R_1 = 3V} \quad (2)$$

Node "b"

$$\boxed{i_1 + i_2 = i_3} \quad (3)$$

We have now 3 equations relating 3 unknown quantities.

Using the given values for R_1 and R_2 , we obtain:

$$\text{From (1): } -i_2 \times 4\Omega - 2i_3 = 2\Omega = 0$$

$$\Rightarrow i_3 = -i_2 \quad (4)$$

$$\text{From (2): } -i_2 \times 4\Omega + 2i_1 = 3\text{Volts}$$

$$\Rightarrow -i_2 + i_1 = \frac{3}{4}\text{ Amp.}$$

OR

$$i_1 = \frac{3}{4}\text{ Amp} + i_2 \quad (5)$$

Replacing (4) and (5) in (3) we obtain

$$\underbrace{\left(\frac{3}{4}\text{ Amp} + i_2\right)}_{i_1} + i_2 = \underbrace{(-i_2)}_{i_3}$$


$$\Rightarrow \frac{3}{4}\text{ Amp} + 2i_2 = -i_2 \Rightarrow \boxed{i_2 = -0.25\text{ Amp}}$$

Also

$$i_1 = \frac{3}{4} A + i_2 = \frac{3}{4} A + (-0.25 A) \Rightarrow \boxed{i_1 = 0.5 \text{ Amp}}$$

And
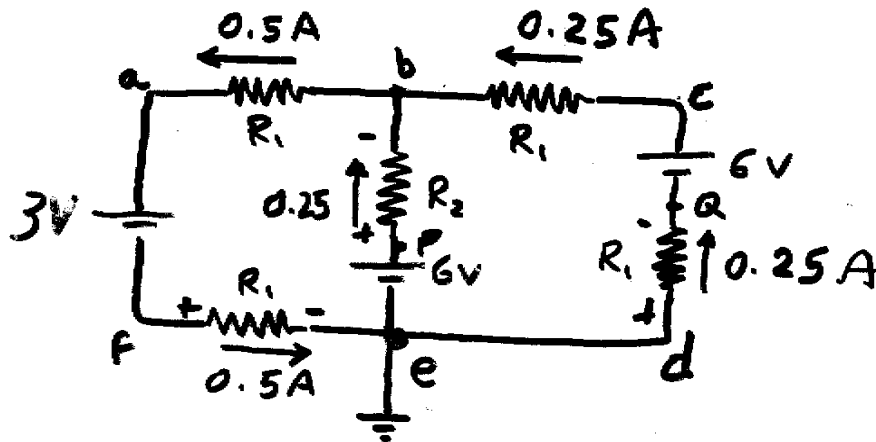
$$i_3 = -i_2 = -(-0.25 \text{ Amp}) \Rightarrow \boxed{i_3 = 0.25 \text{ Amp}}$$




$$R_1 = 2 \Omega$$

$$R_2 = 4 \Omega$$

In the previous circuit we have grounded the node "e". $V_e = 0$

QUESTION: $V_b = ?$; $V_c = ?$; $V_a = ?$

Electric POWER of a battery

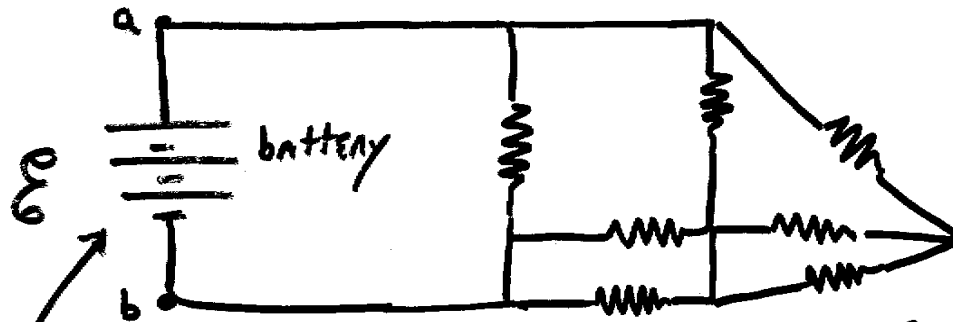


Its job is to maintain the electric potential difference between a and b constant, no matter what

\mathcal{E} is called "electromotive force"

If $\mathcal{E} = 12$ volts for example, the battery will try to keep the potential difference between a and b equal to 12 volts

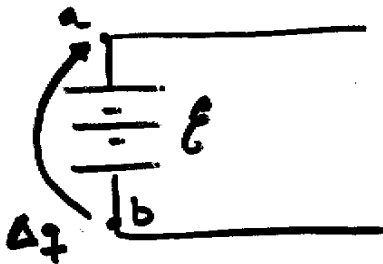(in reality, because any real battery has an intrinsic internal resistance, the above statement is followed approximately)



To take an amount of charge Δq from a potential V_b to V_a the battery has to do a work ΔW equal to

$$\Delta W = \Delta q \times \underbrace{(V_a - V_b)}_{\mathcal{E}}$$

$$\Delta W = \Delta q \times \mathcal{E}$$

Since $i = \frac{\Delta q}{\Delta t}$, we have

$$\frac{\Delta W}{\Delta t} = i \mathcal{E}$$

Work done by the battery per unit time. We call it power

$$P = i \mathcal{E}$$

units:

i ampere

\mathcal{E} volts


P watt = $\frac{\text{Joule}}{\text{sec}}$

Power dissipated in a RESISTOR



An amount of charge Δq starts at a high electric-potential V_a and ends up at lower electric-potential V_b . The energy lost in this process is electric potential
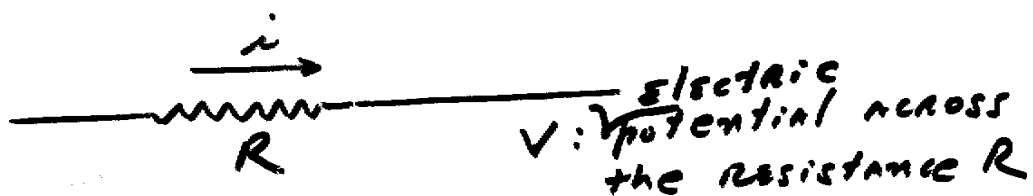
$$\Delta E_{\text{lost}} = \Delta q \cdot \underbrace{(V_a - V_b)}_{\text{let's call it } V}$$



$$\Delta E_{\text{lost}} = \Delta q \cdot V$$

Again, since $i = \Delta q / \Delta t$ we obtain

$$\frac{\Delta E_{\text{lost}}}{\Delta t} = i V$$

Energy dissipated in the resistor per unit time

$$P_{\text{lost}} = i V$$

For a resistance $V = i R$,

$$P_{\text{lost}} = i^2 R$$




i : amperes

R : ohm


P_{lost} : Watt = $\frac{\text{joule}}{\text{sec}}$

charging a capacitor

①

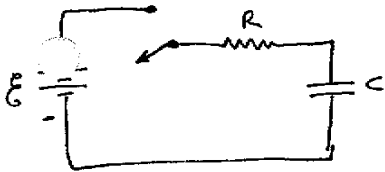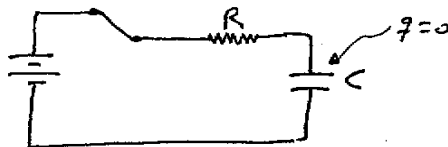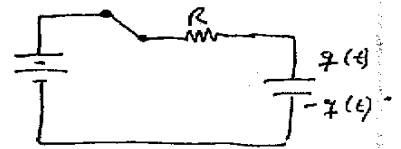At $t = 0$ At $t > 0$ 

$$q(t) = CE(1 - e^{-t/RC})$$

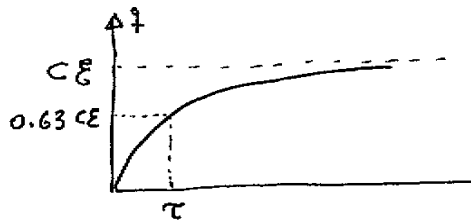for $t \geq 0$ Defining $\tau \equiv RC$ called "time constant"

$$q(t) = CE(1 - e^{-t/\tau})$$

When $t = \tau$

$$q(\tau) = 0.63$$

Problem 46 E, CH-28 (p. 656)RC series circuit. $\mathcal{E} = 12$ volts, $R = 1.4 \times 10^6 \Omega$, $C = 1.8 \mu\text{F}$

a) $\tau = RC = (1.4 \times 10^6 \Omega)(1.8 \mu\text{F}) = 2.52$ seconds

b) max charge on the capacitor: $q_{\text{max}} = CE = q(t) = q_{\text{max}}(1 - e^{-t/\tau})$

$$q_{\text{max}} = (1.8 \times 10^{-6} \text{F})(12 \text{ volts}) = 21.6 \mu\text{C}$$

c) Find the time t for which $q = 16 \mu\text{C}$

$$16 \mu\text{C} = q(t) = 21.6 \mu\text{C} (1 - e^{-t/\tau})$$

$$\Rightarrow 0.74 = 1 - e^{-t/\tau}$$



$$e^{-t/\tau} = 0.26$$

$$-\frac{t}{\tau} = -1.347$$

$$t = 1.347 \tau$$

$$= 1.347 \times 2.52 \text{ second}$$

$$t = 3.4 \text{ sec}$$

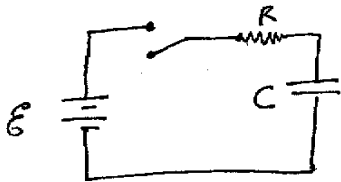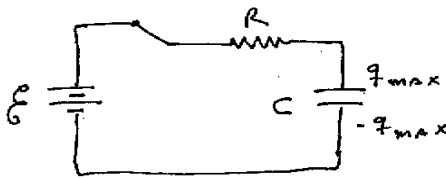Problem 50PAt $t = \infty$ 

- Energy stored in the capacitor:

$$U_c = \frac{1}{2} \frac{q_{\max}^2}{C} = \frac{1}{2C} (\mathcal{E}C)^2 = \boxed{\frac{1}{2} C \mathcal{E}^2 = U_c}$$

Energy stored

- Energy supplied by the battery E_{input}

$$\int_{t=0}^{\infty} \frac{\Delta W}{\Delta t} dt = \int_0^{\infty} P(t) dt = \int_0^{\infty} \mathcal{E} i(t) dt$$

$$\left(\begin{aligned} q(t) &= q_{\max} (1 - e^{-t/RC}) & q_{\max} &= \mathcal{E}C \\ i(t) &= \frac{dq}{dt} = q_{\max} \times (-1) e^{-t/RC} \cdot \left(-\frac{1}{RC}\right) \\ i(t) &= \frac{q_{\max}}{RC} e^{-t/RC} = \frac{\mathcal{E}}{R} e^{-t/RC} \end{aligned} \right.$$

$$E_{\text{input}} = \int_0^{\infty} \mathcal{E} \cdot \frac{\mathcal{E}C}{RC} e^{-t/RC} dt = \frac{\mathcal{E}^2 C}{R} \int_0^{\infty} \frac{e^{-t/RC}}{RC} dt$$


$$\left(\text{Notice } \frac{d}{dt} e^{-t/RC} = -\frac{1}{RC} e^{-t/RC} \right.$$

$$E_{\text{input}} = \mathcal{E}^2 C \left[-e^{-t/RC} \right]_0^{\infty} = \mathcal{E}^2 C [0 + 1]$$

$$\boxed{E_{\text{input}} = \mathcal{E}^2 C} \text{ energy provided by the battery}$$

continuation Problem 50 P

(3)

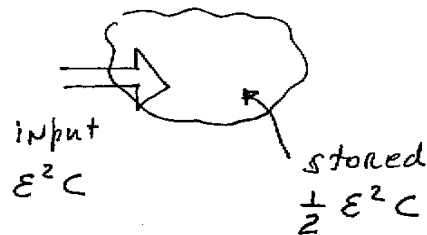

where did the rest of the energy go?

Amount of heat dissipated in the resistor.

$$\text{Heat} = \int_0^{\infty} i^2 R dt = \frac{E^2}{R^2} \int_0^{\infty} e^{-2t/RC}$$

$$= \int_0^{\infty} \left(\frac{E}{R} e^{-t/RC} \right)^2 R dt = \int_0^{\infty} \frac{E^2}{R^2} e^{-2t/RC} R dt$$


$$= \frac{E^2 C}{2} \int_0^{\infty} \frac{2 \times 1}{RC} e^{-2t/RC}$$

Notice $\frac{d}{dt} \left[-e^{-\frac{2}{RC}t} \right] = \frac{2}{RC} e^{-2t/RC}$

$$\frac{E^2 C}{2} \left[-e^{-\frac{2}{RC}t} \right] =$$



$$\text{Heat} = \frac{E^2 C}{2} \left[-e^{-\frac{2}{RC}t} \right] \Big|_0^{\infty} = \frac{E^2 C}{2} [(-0) - (-1)] = \frac{1}{2} E^2 C$$
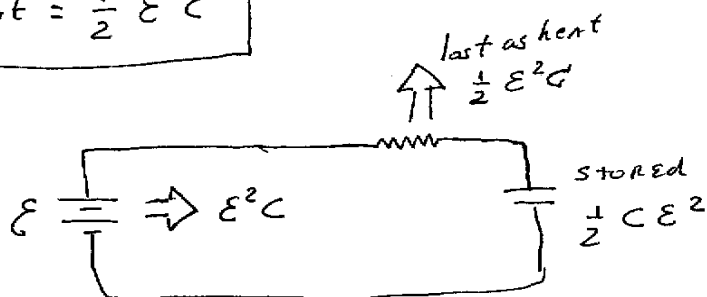
$$\boxed{\text{Heat} = \frac{1}{2} E^2 C}$$



①

Discharging a capacitor

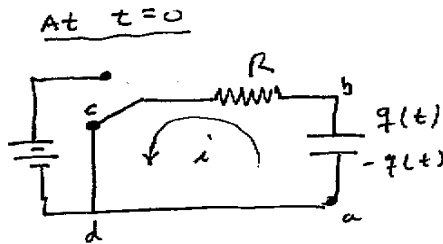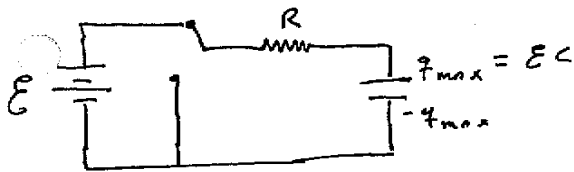

loop abcd

$$\frac{q}{C} - Ri = 0$$


Notice:

If we set $i = \frac{dq}{dt}$

we obtain: $\frac{q}{C} - R \frac{dq}{dt} = 0$


$$\frac{dq}{dt} = \frac{1}{RC} q$$

solution $q(t) = e^{\frac{1}{RC}t}$

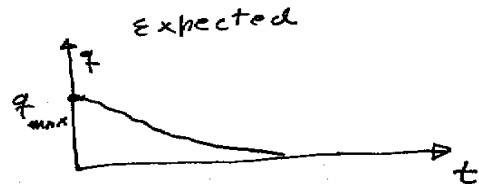

grows as a function of time } something must be wrong

What is wrong?

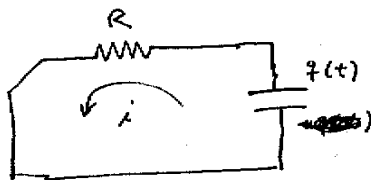

Once we solve this circuits, we anticipate, by physics arguments, that all the quantities in the graph should turn out to be positive

$q(t)$ positive

$i(t)$ positive

(because the capacitor is discharging)

But, when we say

$$i(t) = \frac{dq}{dt}$$

$i(t)$ would turn out to be negative

So, $i = \frac{dq}{dt}$ is not exactly true.

the correct expression ~~is~~ in this case is: $i = - \frac{dq}{dt}$

So, ϵ

$$\frac{q}{C} - Ri = 0$$

$$\Rightarrow \boxed{\frac{q}{C} + R \frac{dq}{dt} = 0}$$

capacitor
discharging

$$\frac{dq}{dt} + \frac{1}{Rc} q = 0 \Rightarrow q(t) = B e^{-at}$$

$$\frac{dq}{dt} = -aB e^{-at}$$

$$-aB e^{-at} + \frac{1}{Rc} B e^{-at} = 0$$


$$(-a + \frac{1}{Rc}) B e^{-at} = 0 \Rightarrow \boxed{a = \frac{1}{Rc}}$$

$$q(t) = B e^{-t/Rc}$$

$$\text{At } t=0 \quad q(0) = q_{\max} = \epsilon C$$

$$\epsilon C = q(0) = B \Rightarrow \boxed{B = \epsilon C}$$


$$\boxed{q(t) = \epsilon C e^{-t/Rc}}$$

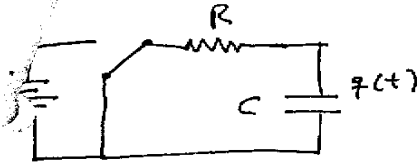

$$q(t) = \mathcal{E}C e^{-t/RC}$$

$$\tau = RC$$

$$q(t) = \mathcal{E}C e^{-t/\tau}$$

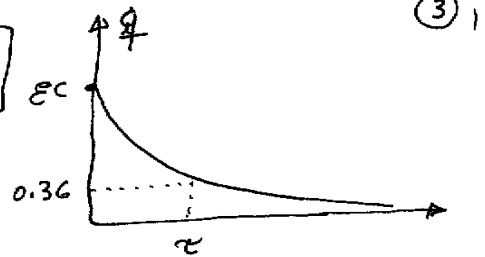

When $t = \tau$

$$q(\tau) = \mathcal{E}C \cdot e^{-1} = 0.36 \mathcal{E}C$$

$$i(t) = - \frac{dq}{dt}$$

$$= - \frac{d}{dt} (\mathcal{E}C e^{-t/RC})$$

$$= \frac{\mathcal{E}C}{RC} e^{-t/RC} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$i(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

