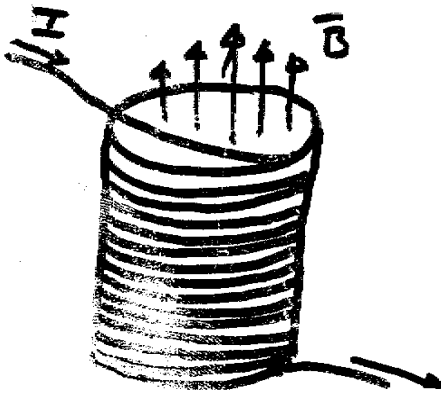


SELF INDUCTANCE (see also p. 725)



INDUCTOR

$$d\vec{A} \uparrow \vec{B} \cdot d\vec{A}$$

The current I produces a magnetic field \vec{B} that varies from point to point, but \vec{B} is proportional to I at every point.

Therefore

The magnetic flux Φ_m is also proportional to I


$$\Phi_m = L I$$



self inductance of the coil

When a current $I(t)$ is changing with time, an electromotive force \mathcal{E} will be induced across the terminals

$$\mathcal{E} = - \frac{d\Phi_m}{dt}$$

$$\mathcal{E} = - \frac{dI}{dt}$$

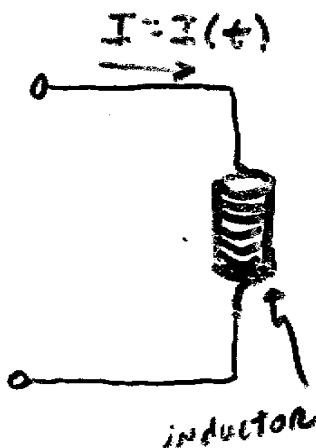

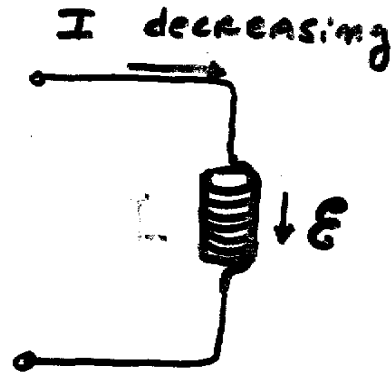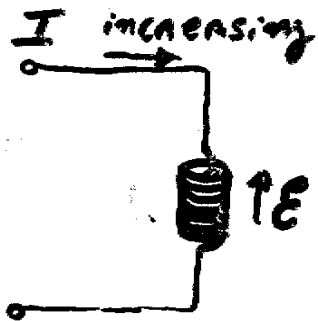

$$\mathcal{E} = -L \frac{dI}{dt}$$

↑
Volts

↑
Henry
[H]

↑
Amp/sec

UNITS of the
self inductance.
L

OR

$$\Phi_m = L I$$





↑
Henry
[H]

↑
Ampere

Since the wire that makes up the coil has some resistance, a REAL inductor (a solenoid is an inductor) is typically represented as
ideal inductor + resistor = real inductor.

What is the effect of an inductor in a circuit?

RL circuit

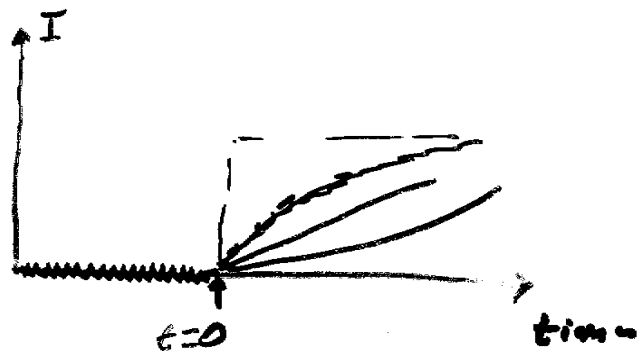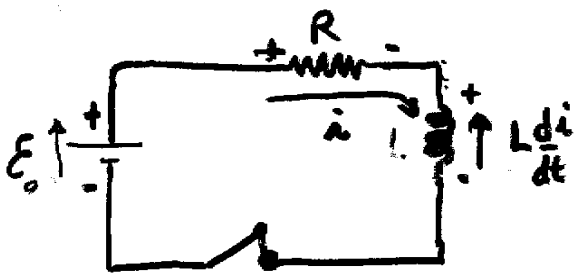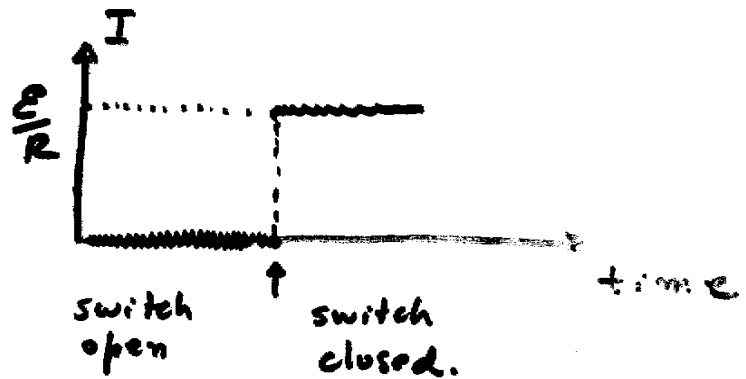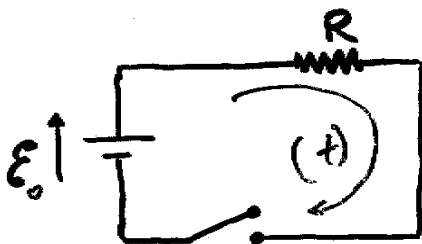

When the switch is closed, Kirchhoff's law indicates.

$$+\mathcal{E}_0 - iR - L \frac{di}{dt} = 0$$

← (\mathcal{E} is a constant in this particular case)

differential equation.

$$L \frac{di}{dt} + iR = \mathcal{E}_0$$

① $i = ?$

Let's try some solutions.

Is $i_1 = \frac{\mathcal{E}_0}{R}$ a solution? ✓

Well, we have to find a more general solution, one that involves ...

We remember that: IF i_1 is a solution and i_2 is another solution of the same linear differential equation, THEN $i_1 + i_2$ is another solution.

So, let's try

$$i = \underbrace{\frac{\mathcal{E}}{R}}_{i_1} + \underbrace{Ae^{-bt}}_{i_2} \quad \begin{array}{l} A, b \text{ are constants,} \\ \text{so far unknown} \end{array} \quad (2)$$

In order to replace (2) in (1) we calculate first:

$$\frac{di}{dt} = -Abe^{-bt}$$

$$iR = \mathcal{E} + RAe^{-bt}$$

thus, replacing these values in (1) we obtain

$$\underbrace{-Abe^{-bt}} + \underbrace{\mathcal{E} + RAe^{-bt}} = \mathcal{E}$$

$$Ab e^{-bt} = RA e^{-bt}$$

$$\Rightarrow \boxed{b = \frac{R}{L}}$$

What about A?

So far, our solution looks like:

$$i = \frac{\mathcal{E}}{R} + A e^{-(R/L)t} \quad \text{solution}$$

"A" will be determined by the "initial conditions"


When $t=0$, $i=0$

$$0 = \frac{\mathcal{E}}{R} + A \underbrace{e^{-(R/L) \cdot 0}}_{=1} \Rightarrow \boxed{A = -\frac{\mathcal{E}}{R}}$$

thus,



$$i = \frac{\mathcal{E}}{R} \left(1 - e^{-(R/L)t} \right)$$

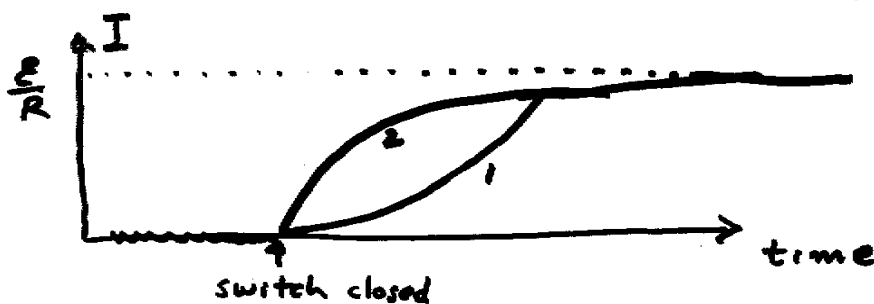where t starts to count just after the switch is closed



* Checkpoints

①

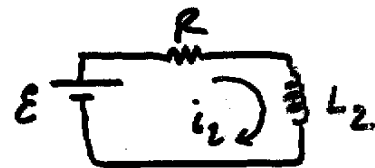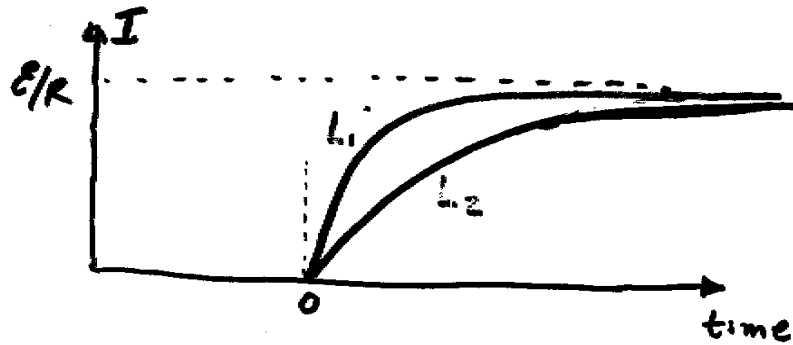

Which self inductance is higher? L_1 or L_2 ?

It is usual to define


$$\tau = \frac{L}{R} \leftarrow \text{"inductive time constant"}$$

The current on a LR circuit can, then, be expressed as

$$i = \frac{E}{R} [1 - e^{-t/\tau}]$$

* Checkpoint: Show that the quantity $\frac{L}{R}$ has units of time

* Checkpoint


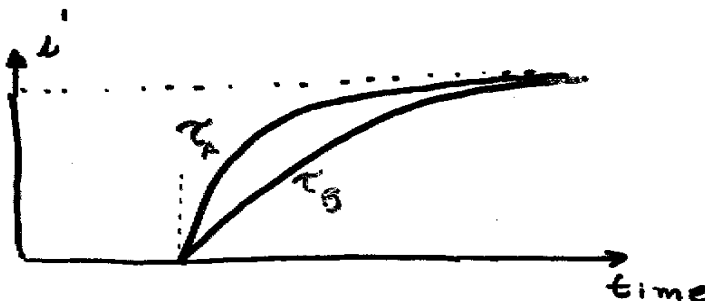


$$\tau_A > \tau_B$$

$$\tau_A = \tau_B$$

$$\tau_A < \tau_B \quad \checkmark$$

Interpretation of τ

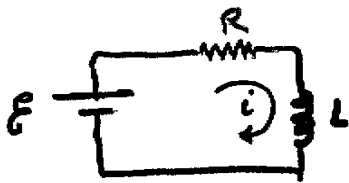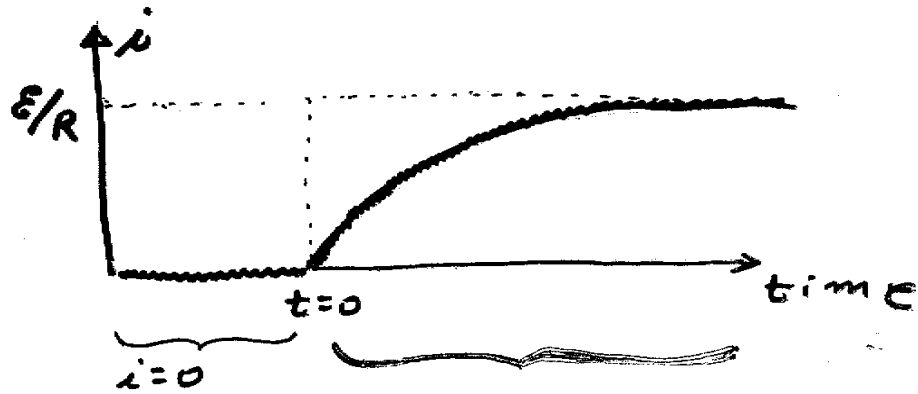


$$i(t) = \frac{E}{R} [1 - e^{-t/\tau}]$$

$$\text{where } \tau = \frac{L}{R}$$



$$\text{When } t = \tau = \frac{L}{R}$$
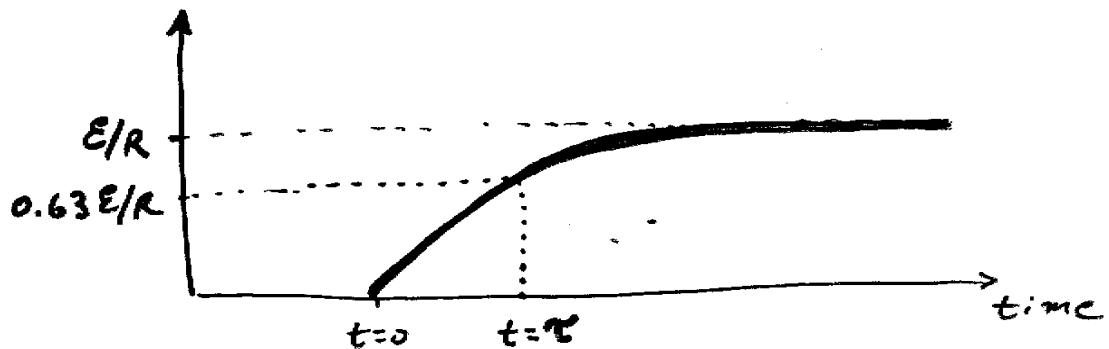
$$i(\tau) = \frac{E}{R} [1 - e^{-\tau/\tau}] = 0.63 \frac{E}{R}$$





Physical interpretation

Big "L" \Rightarrow

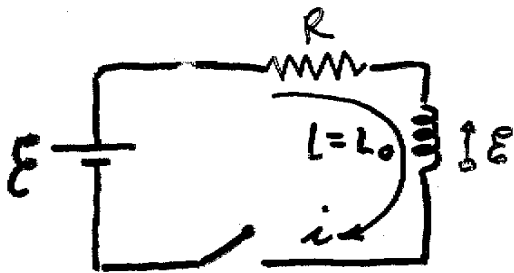
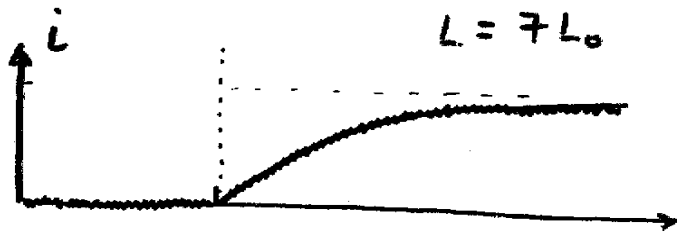


$$\mathcal{E} = -L \frac{di}{dt}$$

Low "L" \Rightarrow

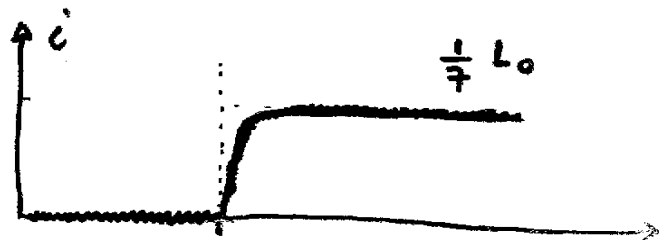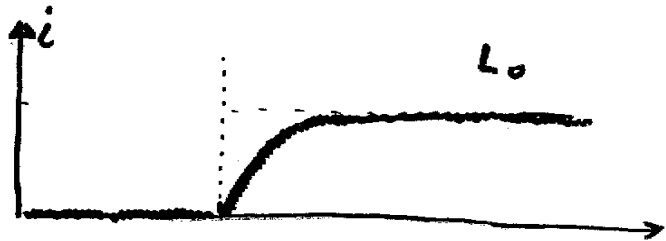

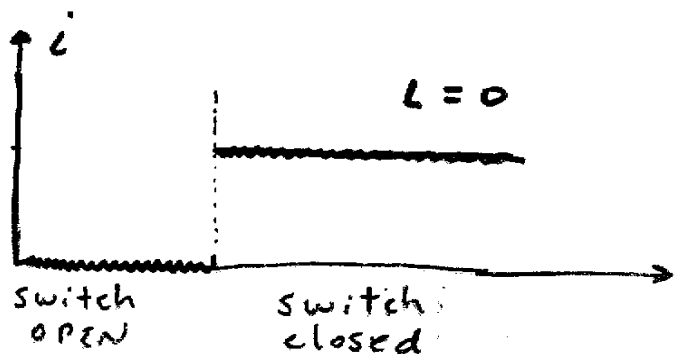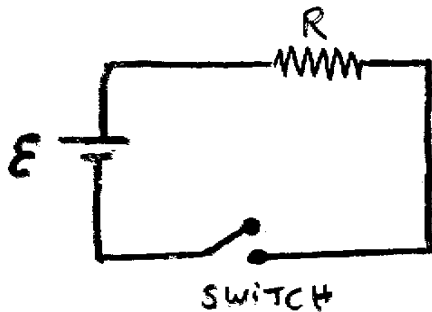L_0 acts as a brake that opposes any change in the current. The lower L , the less opposition to the current variation.



MAGNETIC ENERGY STORED IN A INDUCTOR


We know


$$\mathcal{E}_0 = iR + L \frac{di}{dt}$$

Let's multiply this equation
by i :

$$i\mathcal{E}_0 = i^2 R + i \frac{dL}{dt}$$
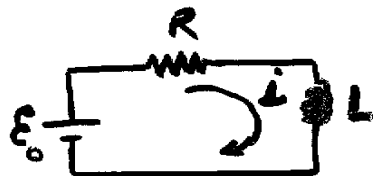
$$i\mathcal{E}_0 = i^2 R + \frac{1}{2} L \frac{di^2}{dt}$$



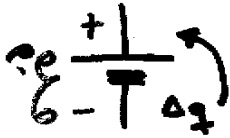

work done on a charge Δq to take it across a potential difference \mathcal{E} is:

$$(\Delta q) \mathcal{E}.$$

If it does it in a time Δt , then the rate at which the battery does work on the circuit is:

$$\frac{\Delta q \mathcal{E}}{\Delta t}$$

$$i \mathcal{E}$$



$$i^2 R$$

Rate at which energy is dissipated through the resistor R as Thermal Energy

$$\frac{1}{2} L \frac{di^2}{dt}$$

CONSERVATION OF ENERGY indicates that this term corresponds to the rate at which the magnetic energy is being stored in the inductor.

This is to say:

$$\frac{dU}{dt} = \frac{1}{2} L \frac{di^2}{dt}$$

$$U = \frac{1}{2} L i^2$$




MAGNETIC ENERGY
stored in the
inductor.

Self-inductance L

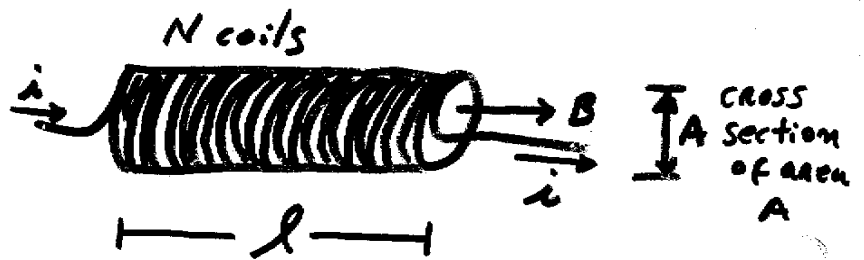Question:

What is the selfinductance L of a
solenoid?



$$n = \frac{N}{l} \text{ \# of turns per unit length}$$

We already know that

$$B = \mu_0 \frac{N}{l} i \quad ; \quad l \gg A$$


The total magnetic flux through the
 N coils is

$$\Phi = N B A$$

$$= \mu_0 \frac{N^2}{l} A i$$

$$B = \mu_0 \frac{N^2}{l} A$$

of a solenoid

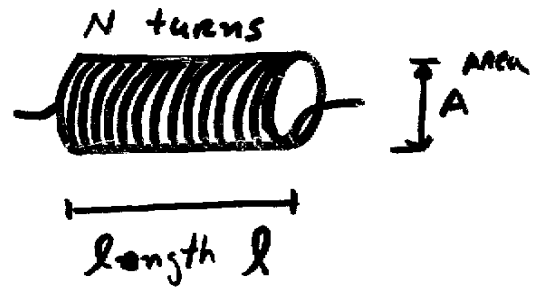

QUESTION: What is the magnetic energy stored in a solenoid carrying a current i ?

$$U = \frac{1}{2} i^2$$

$$= \frac{1}{2} \left(\mu_0 \frac{N^2}{l} A \right) \frac{B^2}{\left(\mu_0 \frac{N}{l} \right)^2}$$


$$= \frac{1}{2} Al \frac{B^2}{\mu_0}$$

(Notice that Al is the volume of the solenoid)

$$\mu_B = \frac{B^2}{2\mu_0}$$

MAGNETIC ENERGY
density (Joules/m³)

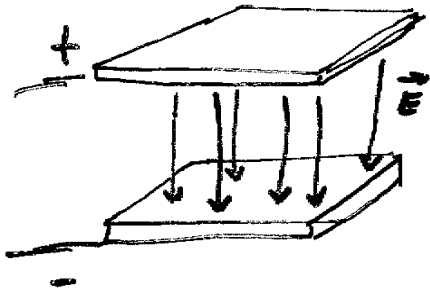
Remember, earlier we found that energy is stored in the electric field



$$U_E = \frac{\text{ENERGY}}{\text{Volume}}$$

$$= \frac{1}{2} \epsilon_0 E^2$$

Now, we just realized that

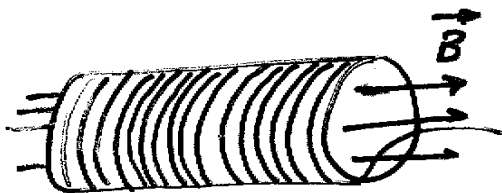

$$U_m = \frac{1}{2\mu_0} B^2$$

$$\frac{1}{4\pi\epsilon_0} = 9 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}$$

$$\frac{\mu_0}{4\pi} = 10^{-7} \frac{\text{Tm}}{\text{Amp}}$$


Whenever there exist an electro-magnetic field, there exist an electromagnetic energy density given by

$$u = \frac{\text{electromagnetic energy}}{\text{volume}} = \frac{1}{2} \epsilon_0 E^2 + \frac{1}{2\mu_0} B^2$$

u is in $\frac{\text{Joules}}{\text{m}^3}$

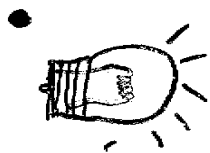EXERCISE: Just for curiosity, find the value of

$$\frac{1}{\sqrt{\epsilon_0 \mu_0}} \quad \text{in MKS}$$



light
→

what is the speed of light? (in m/s)

* checkpoint #6, page 729.

* checkpoint

At $t = t_1$, the switch is closed. Later, at $t = t_2$ the switch is opened again.

Make an sketch of i vs time.

